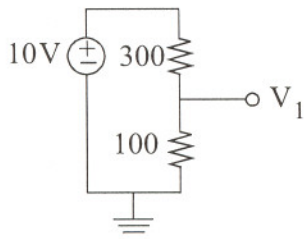


Problem 1 – Short Answers (20 points)


[2 pts.] (a)



$$10 \cdot \frac{100}{100+300} = 2.5V$$

$$V_1 = 2.5V$$


[2pts.] (b)

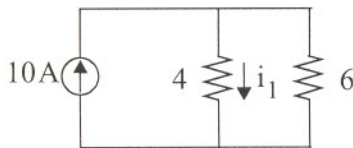

$$10 \cdot \frac{6}{4+6} = 6 \text{amps}$$

$$i_1 = 6A$$


[2 pts.] (c)

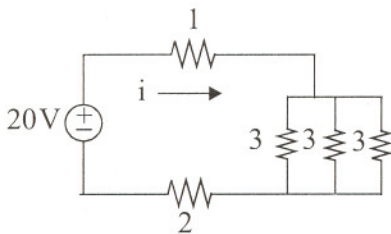

$$\frac{20V}{1 + \frac{3}{3} + 2} = 5 \text{amps}$$

$$i = 5A$$

[4 pts.] (d)

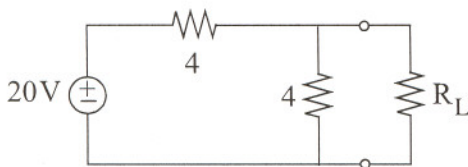

For what value of R_L is power in R_L maximized?

$$R_L = 2\Omega \quad 2\Omega$$

What is the maximum power dissipated in R_L ?

$$12.5 \text{ watts}$$


$$i = \frac{10V}{4\Omega}, P = i^2 R$$

$$P = \frac{100}{16} \cdot 2 = 12.5 \text{ watts}$$

Thev Equiv



Problem 1 (cont.)

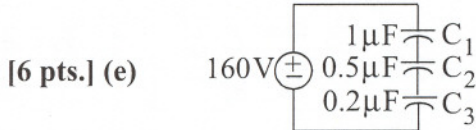

Determine charge (q) and voltage across each capacitor.

$$q_1 = 2 \times 10^{-5} \text{ C}$$

$$V_1 = 20 \text{ V}$$

$$q_2 = 2 \times 10^{-5} \text{ C}$$

$$V_2 = 40 \text{ V}$$

$$q_3 = 2 \times 10^{-5} \text{ C}$$

$$V_3 = 100 \text{ V}$$

$$q_1 = q_2 = q_3$$

$$C_1 V_1 = C_2 V_2 = C_3 V_3$$


$$V_1 + V_2 + V_3 = 160 \text{ V}$$

$$q \cdot \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = 160 \text{ V}$$

$$q = \frac{160 \text{ V}}{10^6 (1 + 2 + 5)} = 20 \times 10^{-6} \text{ C}$$

[4 pts.] (f) Short Question

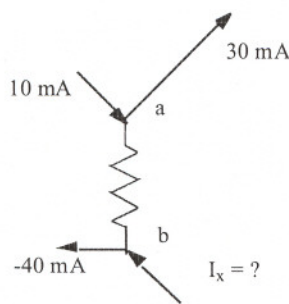Here is a circuit fragment – a 100-ohm resistor imbedded in a very large circuit that provides the currents shown here. Find the unknown current I_x and the voltage V_{ab} across the resistor.




$$I_x = \underline{\hspace{2cm}}$$

$$V_{ab} = \underline{\hspace{2cm}}$$

$$10 \text{ mA} - 30 \text{ mA} - (-40 \text{ mA}) + I_x = 0$$

$$I_x = -20 \text{ mA}$$

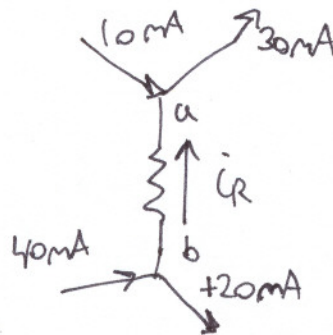


$$i_r = 20 \text{ mA}$$

$$V_{ab} = -100 \cdot 20 \text{ mA}$$

$$= -2 \text{ V}$$

Problem 2 (20 points)

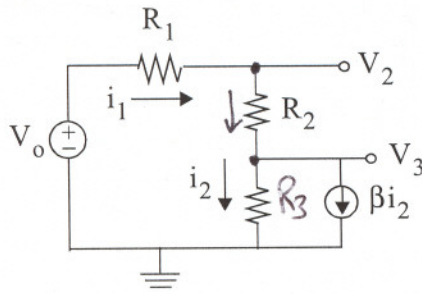

$V_0, R_1, R_2, R_3, \beta$ are known.


- [10 pts.] (a) Write (but do not solve) a minimum set of equations that could be solved for unknowns V_2 and V_3 using Kirchhoff's Current Law, KCL. (Equations in box for full credit.)

$$\begin{aligned} \text{at } V_2: \quad & \frac{V_0 - V_2}{R_1} - \frac{(V_2 - V_3)}{R_2} = 0 \\ \text{at } V_3: \quad & \frac{V_2 - V_3}{R_2} - \frac{V_3}{R_3} - \beta \frac{V_3}{R_3} = 0 \end{aligned}$$

- [10 pts.] (b) Write (but do not solve) a minimum set of equations that could be solved for unknowns i_1, i_2 using Kirchhoff's Voltage Law (KVL). (Equations in box for full credit.)

$$\begin{aligned} V_0 - i_1 R_1 - i_1 R_2 - i_2 R_3 &= 0 \quad (\text{KVL around loop}) \\ i_1 - i_2 - \beta i_2 &= 0 \quad (\text{KCL at node 2}) \end{aligned}$$

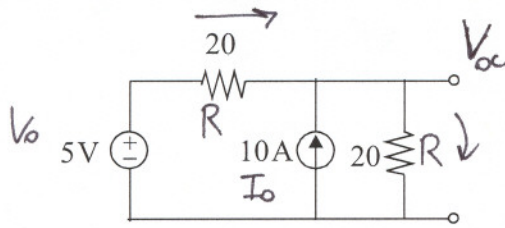Problem 3 – Equivalent Circuits (20 points)




$$\frac{V_0 - V_{oc}}{R} + I_0 - \frac{V_{oc}}{R} = 0$$

$$V_0 + I_0 R = 2V_{oc}$$

$$V_{oc} = \frac{V_0 + I_0 R}{2}$$

$$I_{sc} = \frac{V_0}{R} + I_0$$

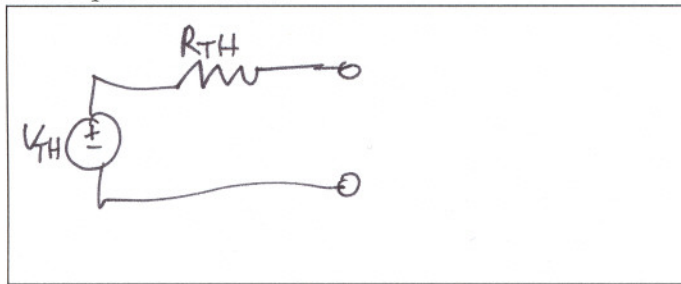[2 pts.] (a) Draw the Thévenin equivalent circuit.



$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{1}{2}(V_0 + I_0 R)}{\frac{1}{R}(V_0 + I_0 R)} = R/2$$


$$V_{TH} = V_{oc} = \frac{5 + 20 \cdot 10}{2} = 102.5V$$

[14 pts.] (b)

$$R_{TH} = 10 \Omega$$

$$V_{TH} = 102.5V$$

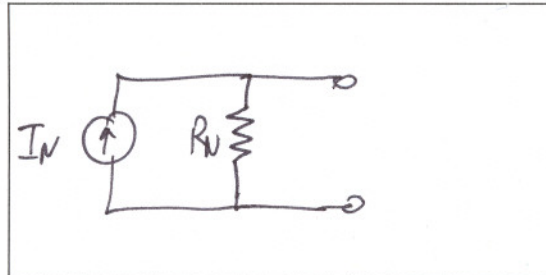[2 pts.] (c) Draw the Norton equivalent circuit.



[2 pts.] (d) In general, if you know V_{TH} and R_{TH} , how do you determine R_N and I_N ?

$$R_N = R_{TH}$$


$$I_N = V_{TH} / R_{TH}$$

Problem 4 – Lab Related Question (18 points)


Suppose you buy a strange-looking battery at the Berkeley Surplus Center and want to find its Thévenin equivalent circuit experimentally. You have a multimeter with voltage, current and resistance scales, and you also have one resistor R , one capacitor C , and one inductor L . Incidentally, you don't want to short circuit the battery – it would be bad for it!

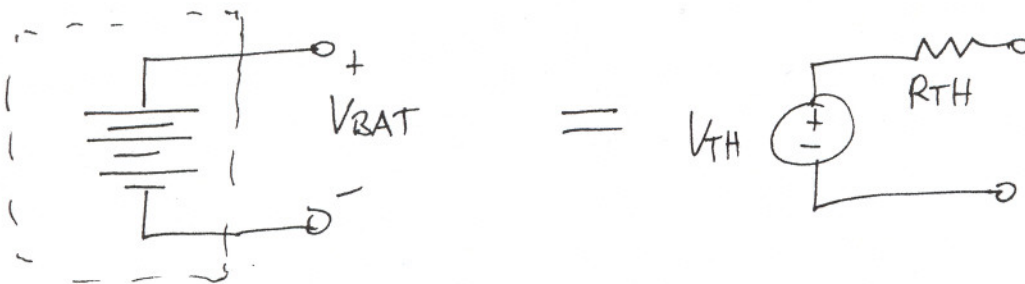- a) How can you find V_{Th} safely?
- b) How can you find R_{Th} safely?


Draw the circuits showing how you'd connect the meter, the battery and any other components, and write any equations you will use in the process,



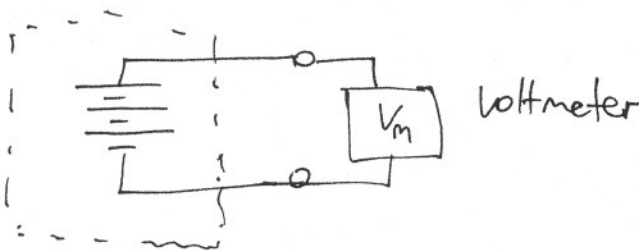
a) open circuit voltage $V_{BAT} \equiv V_{TH}$. So just use multimeter voltage scale.



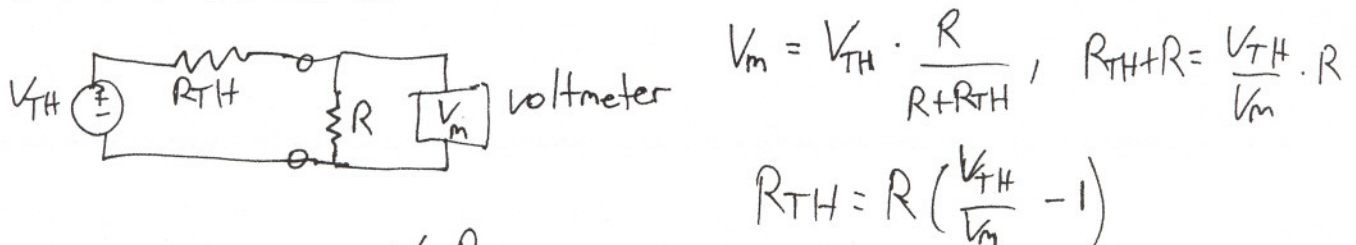b) We know $R_{TH} = \frac{V_{TH}}{I_{sc}}$, but we don't want to measure short circuit current. We can use known R + voltmeter to find R_{TH} :



[if you use ~~an~~ a capacitor ^{w/o R} you instantly ~~casly~~ short V_{BAT}].

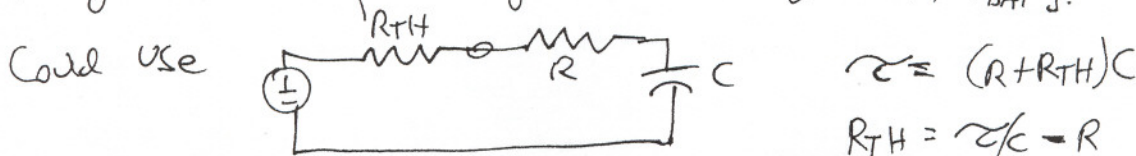

Problem 5 – RL Circuit

An RL circuit with a voltage source and a very fast-acting switch is shown. The values of the components are: $V_s = 2\text{ V}$; $R_1 = 20\Omega$; $R_2 = 980\Omega$; $L = 0.1\text{ H}$. At time $t = 0$, a long time after the switch has closed, the switch opens.

[2 pts.] (a) What is the current i_L that is flowing at time $t = -2\text{ s}$?

$$i_L(-2) = 0.1\text{ A}$$

$$\frac{V_s}{R_1} = \frac{2}{20} = 0.1\text{ amp}$$

[2 pts.] (b) What is the time constant for the RL circuit?

$$\tau = 10^{-4}\text{ sec}$$


after switch opens $\tau = \frac{L}{R_1 + R_2}$
 $= \frac{0.1}{20 + 980} = 10^{-4}\text{ sec}$

[6 pts.] (c) Write KVL for time $t = 0^+$.

for inductor, current can not change instantaneously. $V_L = L \frac{di}{dt}$
 $-iR_2 - iR_1 - V_L = 0$

[4 pts.] (d) Find the voltage $V_a(t = 0^+)$.
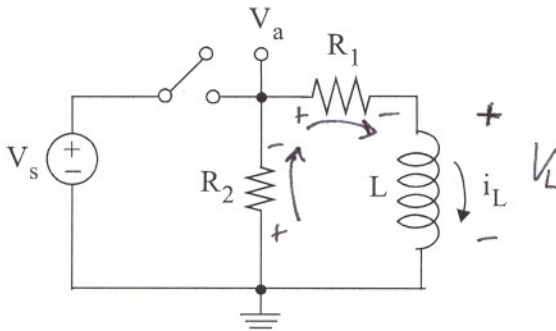
$$= -i_L R_2 = -(0.1)980 = -98\text{ V}$$



$$v_a(t = 0^+) = -98\text{ V}$$

[8 pts.] (e) Determine $v_a(t)$ for $t > 0$.

$$v_a(t) = v_{af} + [v_a(0^+) - v_{af}]e^{-t/\tau}$$

$$v_a(t) = -98e^{-t \cdot 10^4 \text{ sec}^{-1}}$$

$$\lim_{t \rightarrow \infty} v_a(t) = 0$$

$$t \rightarrow \infty \quad v_a(t) = v_a(t=0^+)e^{-tR/L}$$