

Name: _____

SID: _____

Name of student at your left:
_____ (1 point)

Name of student at your right:
_____ (1 point)

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering
and Computer Sciences


B. E. BOSER

Midterm 2
October 26, 2004

EECS 105
FALL 2004

- *Closed book, closed notes.*
- *No calculators.*
- *Copy your answers into marked boxes on exam sheets.*
- *Simplify numerical and algebraic results as much as possible.*
Up to 5 points penalty for results that are not reasonably simplified.
- *Mark your name and SID at the top of the exam and all extra sheets.*
- *Be kind to the graders and write legibly. No credit for illegible results.*

Problem 1 [25 points]

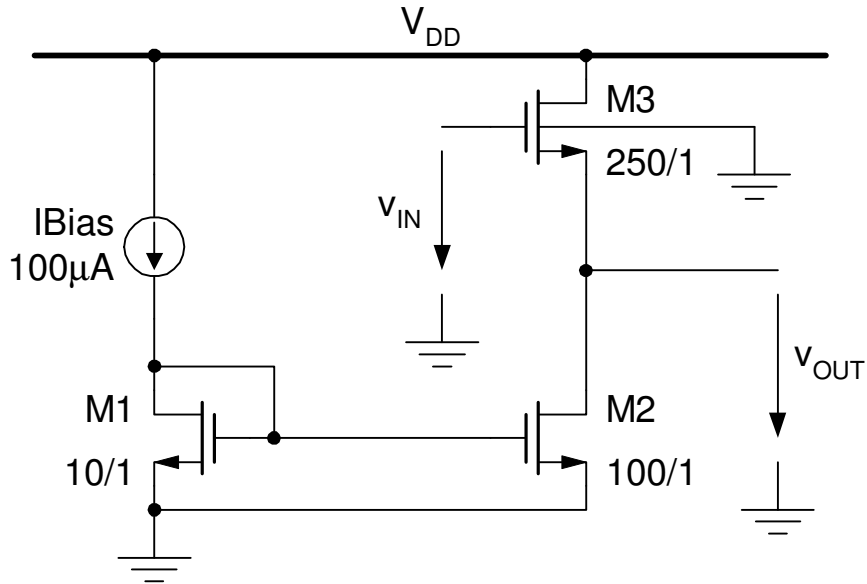

Given: $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$, $\lambda_n = 0.01\text{V}^{-1}$ @ $L = 1\mu\text{m}$
 $g_m r_o \gg 1$
 The circuit is biased such that all transistors are in saturation.

a) [10 points] Find *numerical* values (not expressions) for:


$I_{D3} =$	μA
------------	---------------

$g_{m3} =$	μS
------------	---------------

b) [15 points] Find an *algebraic* expression for the small signal output resistance (at terminal v_{OUT}) of the circuit as a function of transistor small-signal parameters. Use $g_m r_o \gg 1$ to simplify your result as much as possible:

$$r_{out} =$$

Problem 2 [25 points]

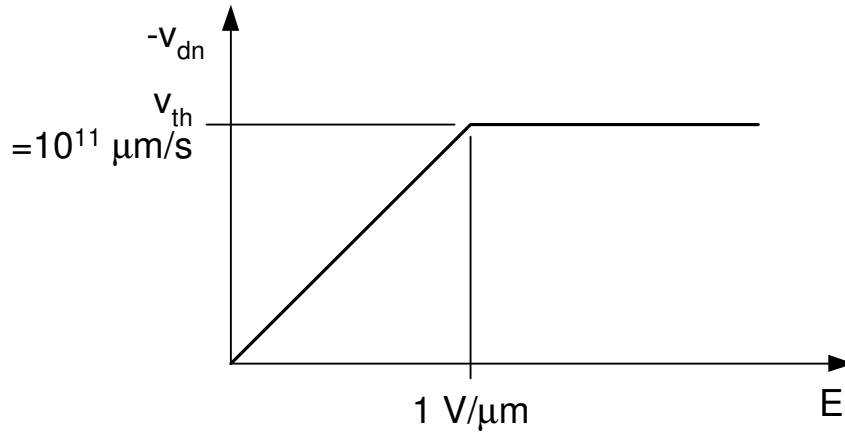

The above sketch shows a rough approximation of the electron drift velocity versus the electrical field in Silicon. For an NMOS transistor with $L=0.1\mu\text{m}$, $W=10\mu\text{m}$, and $C_{ox}=5\text{fF}/\mu\text{m}^2$ calculate the following:


a) [10 points] What is the minimum V_{DS} (*numerical* value) for which current flow is limited by the thermal carrier drift velocity? Assume that the field in the channel is uniform.

$V_{DS} =$	V
------------	-----

b) [15 points] Find the *numerical* value of the maximum drain current I_D for $V_{GS} - V_{TH} = 1V$. Hint: get the current from the channel charge and its velocity.


$I_D =$		mA
---------	--	-------------

Problem 3 [25 points]

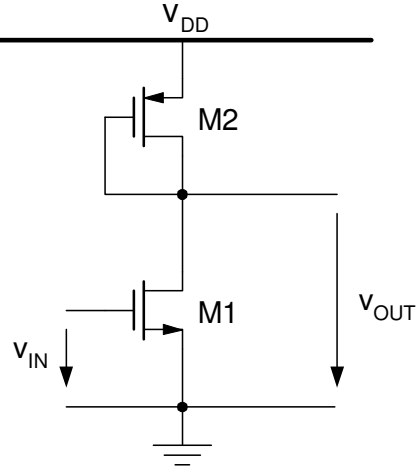


The circuit shown above is biased so that all transistors are in saturation. Draw a small signal model (label all elements with appropriate symbols, e.g. g_{m1} , r_{o2}) and find an *algebraic* expression for the small-signal voltage gain $a_v = v_{out}/v_{in}$ as a function of small-signal parameters (g_m 's and r_o 's). Use $g_m r_o \gg 1$ to simplify your result.

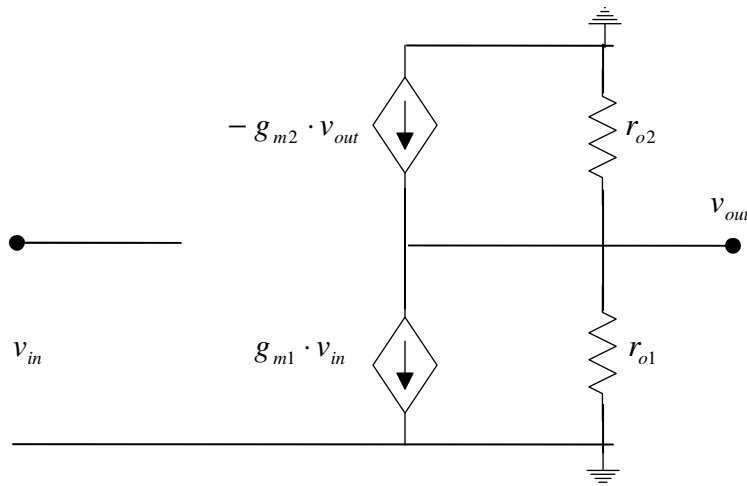Small-signal model (neatness counts) [13 points]:



$a_v =$

Problem 4 [23 points]

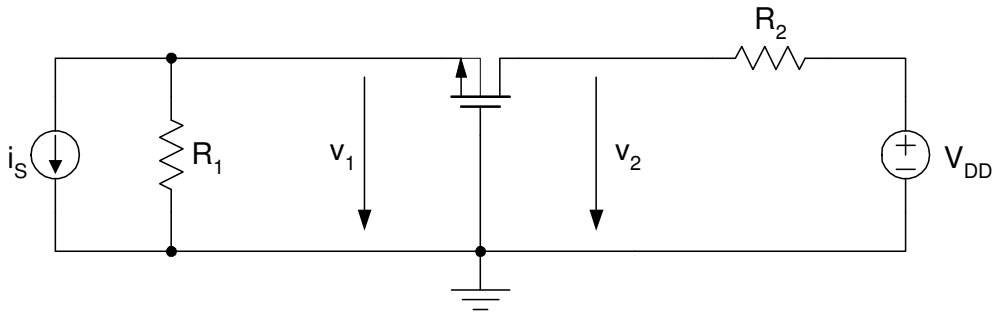

The circuit shown above is biased so that the transistor is in saturation.

a) [8 points] What is the type of this amplifier?

Common _____

b) [15 points] Find an *algebraic* expression for the small-signal voltage ratio v_2/v_1 for $i_s=0$ as a function of R_1 , R_2 , and transistor small-signal parameters.
Hint: you may find small-signal model very helpful to answer this question.

$v_2/v_1 =$