 



Problem 1 [15 points]: Cascodes

- a) What is the advantage of using a BJT (Q_2 , as shown below on the left) rather than a resistor (R_E , as shown below on the right) to achieve a high value of output resistance (R_{out})? [3 pts]

Q_2 provides a large degeneration resistance ($\sim r_{o2}$) without sustaining a large voltage drop (V_{EC2}) as compared with R_E for which the voltage drop $V_E \approx I_{C1} R_E$ can be large if R_E is large. Thus, the use of a BJT rather than a resistor provides for larger headroom for the output voltage signal to swing.



 - b) Suppose a PNP cascode is to be used as a 0.1mA current source, as shown below. What should be the values of the bias voltages V_{b1} and V_{b2} ? Assume that $I_S = 10^{-16}A$ for each BJT, and that the Q_2 collector junction is forward-biased by no more than 0.3V to ensure that Q_2 operates in active mode. $V_{CC} = 2.5V$. Note that $e^{0.72/0.026} \approx 10^{12}$. [8 pts]



In order for $I_{C1} \approx I_{C2} = 0.1 \text{ mA} = 10^{-4} \text{ A}$,

$|V_{BE}|$ for each BJT should be $V_T \ln \left(\frac{I_C}{I_S} \right)$:

$$|V_{BE}| = 0.026 \ln \left(\frac{10^{-4}}{10^{-16}} \right) = 0.026 \ln 10^{12} = 12 \times 0.060 = 0.72 \text{ V}$$


$$V_{b2} = V_{CC} - V_{EB2} = 2.5 \text{ V} - 0.72 \text{ V} = \boxed{1.78 \text{ V}}$$

If the Q_2 collector junction is forward-biased by 0.3V,

$$V_X - V_{b2} = 0.3 \text{ V} \Rightarrow V_X = 0.3 \text{ V} + 1.78 \text{ V} = 2.08 \text{ V}$$

$$V_{b1} \leq V_X - V_{EB1} = 2.08 \text{ V} - 0.72 \text{ V} = \boxed{1.36 \text{ V}}$$

 - c) Suppose that a PNP cascode is to be used as a voltage amplifier, as shown below. Which transistor (Q_1 or Q_2) should be used as the amplifying device? Explain briefly. [4 pts]




Q_2 should be used as the amplifying transistor.

If the input voltage signal is applied to the base of Q_1 , the voltage gain is not as high, due to emitter degeneration.

Problem 2 [15 points]: Current Mirrors

Consider the circuit shown below:

 

a) What is the purpose of the transistor Q_{REF} ? [2 pts]

Q_{REF} generates a bias voltage for the base of the current-mirror transistor Q_1 .

b) Derive an expression for I_{copy} in terms of I_{REF} and m , neglecting the effect of the transistor base currents. [3 pts]

Assuming that $I_{C,REF} = I_{REF}$, $V_X = V_T \ln\left(\frac{I_{REF}}{I_{S,REF}}\right) = V_T \ln\left(\frac{I_{copy}}{I_{S,1}}\right)$

$$\Rightarrow \frac{I_{REF}}{I_{S,REF}} = \frac{I_{copy}}{I_{S,1}} \Rightarrow I_{copy} = \frac{I_{S,1}}{I_{S,REF}} I_{REF}$$

I_S for a BJT is proportional to the emitter area. $\Rightarrow \frac{I_{S,1}}{I_{S,REF}} = \frac{mA_E}{A_E} = m$

$$\Rightarrow \boxed{I_{copy} = m I_{REF}}$$

c) Considering the effect of the transistor base currents, what is the error in I_{copy} ? [8 pts]

Q_{REF} base current is $\frac{I_{C,REF}}{\beta} = \frac{I_{copy}}{m\beta}$; Q_1 base current is $\frac{I_{copy}}{\beta}$

Applying KCL: $I_{REF} = I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} = \frac{I_{copy}}{m} + \frac{I_{copy}}{m\beta} + \frac{I_{copy}}{\beta}$


$$I_{REF} = I_{copy} \left[\frac{1}{m} + \frac{1}{m\beta} + \frac{1}{\beta} \right] = \frac{I_{copy}}{m} \left[1 + \frac{1}{\beta} + \frac{m}{\beta} \right]$$

$$I_{copy} = m I_{REF} \frac{1}{\left[1 + \frac{m+1}{\beta} \right]} \approx m I_{REF} \left(1 - \frac{m+1}{\beta} \right)$$

$$\Rightarrow \text{fractional error is } -\frac{m+1}{\beta}$$

 d) How can the error in I_{copy} be reduced, without changing I_{REF} ? [2 pts]


The error in I_{copy} can be reduced by using another transistor to supply the base currents for Q_{REF} and Q_1 :



In this case, the fractional error is reduced by the factor β , since $I_{B,F} \approx \frac{1}{\beta} (I_{B,REF} + I_{B,1})$.

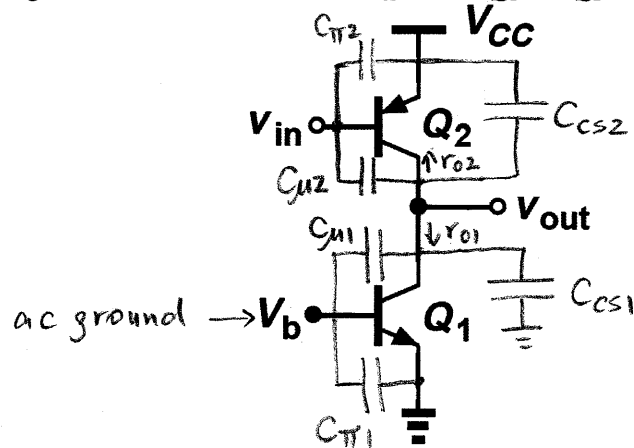Problem 3 [20 points]: Frequency Response

Consider the amplifier stage shown below. Assume that $V_A \neq \infty$ for Q_1 and Q_2 .



- a) Write an expression for the low-frequency voltage gain. [4 pts]

This is a common-emitter stage with " R_C " = $r_{o1} \parallel r_{o2}$:

$$A_v = -g_{m2}(r_{o1} \parallel r_{o2})$$

- b) Why is the voltage gain of this amplifier dependent on the signal frequency? [2 pts]

The BJTs have junction capacitances, whose impedances depend on the signal frequency.

- c) Draw the BJT junction capacitances ($C_{\pi 1}$, $C_{\mu 1}$, C_{CS1} , $C_{\pi 2}$, $C_{\mu 2}$, C_{CS2}) on the circuit diagram above. [6 pts]

- d) Use Miller's theorem to derive an expression for the bandwidth. Assume that the dominant pole is associated with the input node. [6 pts]

The floating capacitance $C_{\mu 2}$ can be converted into a grounded capacitance at the input node $C_{\mu 2}(1 - A_v)$.

The total capacitance seen at the input node is $C_{\pi 2} + C_{\mu 2}(1 - A_v)$.

The resistance seen at the input node is $r_{\pi 2}$.

The pole associated with the input node is $\omega_{p,in} = \frac{1}{r_{\pi 2} [C_{\pi 2} + C_{\mu 2}(1 - A_v)]}$ which is the bandwidth (in units of rad/s)

- e) Considering your answers to parts (a) and (d) above, describe the trade-off between voltage gain and bandwidth. [2 pts]

In order to achieve large voltage gain, g_{m2} should be large.

If g_{m2} is large, then $r_{\pi 2} = \frac{\beta}{g_{m2}}$ is small \Rightarrow bandwidth will be large.

\Rightarrow There is no trade-off between A_v and BW.

(Actually, $\omega_{p,in}$ will not be the dominant pole anymore.)

Problem 4 [15 points]: MOSFETs

a) Consider a long-channel MOSFET with the I - V characteristic as shown below.

i) What is the threshold voltage (V_{TH}) of this device? [2 pts]

From the plot, $V_{Dsat} = 0.5V$.


$$V_{Dsat} = V_{GS} - V_{TH} \Rightarrow V_{TH} = V_{GS} - V_{Dsat} = 0.5V$$

ii) Indicate (by drawing a **dashed curve** on the plot) how the I - V characteristic would change if $V_{GS} - V_{TH}$ were to be decreased by a factor of 2. [3 pts]

V_{Dsat} decreases by 2X

$I_{Dsat} \propto (V_{GS} - V_{TH})^2$ decreases by 4X

λ is unchanged

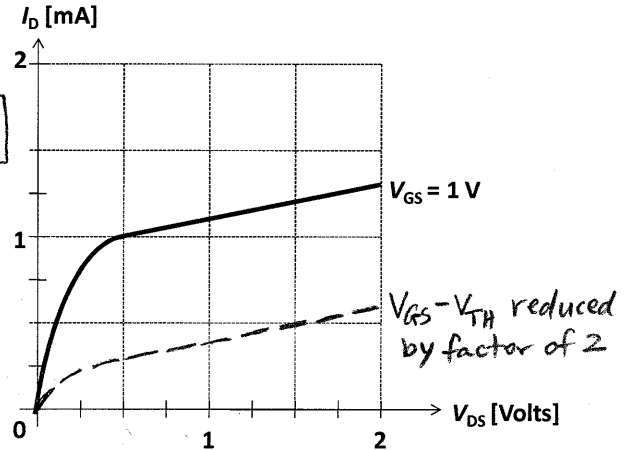

b) Indicate how the small-signal parameters of a long-channel MOSFET would change, if the gate-oxide thickness were to be decreased. Assume $V_{GS} - V_{TH}$ remains the same. Give qualitative explanations for your answers. [6 pts]

MOSFET Parameter	Parameter will (check one)			Brief Justification
	increase	decrease	not change	
Transconductance, g_m	✓			Capacitive coupling of the channel potential to the gate voltage is increased, so V_a will have a stronger influence on I_D
Output resistance, r_o		✓		The channel-length modulation effect is not affected by t_{ox} , i.e. λ does not change. However, I_D increases if t_{ox} increases (for the same reason as above) and so $r_o \approx \frac{1}{\lambda I_D}$ decreases.

c) What is the channel length modulation effect? [2 pts]


The drain current increases with increasing V_{DS} in the saturation region of operation, due to the length of the inversion-layer channel decreasing.

e) Why does the drain current eventually saturate in a short-channel MOSFET, as the drain-to-source voltage (V_{DS}) is increased? [2 pts]

The drain current in a short-channel MOSFET eventually saturates as V_{DS} increases, due to velocity saturation.

 Problem 5 [15 points]: MOSFET Amplifiers

Consider the MOSFET amplifier stage shown below. Assume that $\lambda \neq 0$ for each of the long-channel MOSFETs.



Assume that $\frac{1}{g_m} \ll r_o$ for each MOSFET

- a) What type of amplifier is this [2 pts]? Circle one of the following, and justify your answer:

Common Emitter Common Base Follower Cascode

Input signal is applied to gate of M2.

Output signal is taken from drain of M2.

- b) What is the purpose of transistor M3? [2 pts]

M3 serves as a current source.

- c) What is the purpose of the capacitor C1? [2 pts]

C1 is used to couple the input voltage signal to the gate of the amplifying transistor (M2), without affecting the DC bias.

- d) Derive expressions for the low-frequency voltage gain (A_v), input resistance (R_{in}), and output resistance (R_{out}). [9 pts]

The resistance seen looking into the drain of M2 is approximately

$$g_{m2} r_{o2} \cdot \left(\frac{1}{g_{m1}} \parallel r_{o1} \right)$$

so the total resistance seen looking into the output node is

$$R_{out} = r_{o3} \parallel g_{m2} r_{o2} \left(\frac{1}{g_{m1}} \parallel r_{o1} \right) \approx r_{o3} \parallel r_{o2} \quad \text{since } g_{m1} \approx g_{m2} \text{ (since } I_{D1} = I_{D2} \text{)}$$

Since the resistance looking into the gate of M2 is infinite,

$$R_{in} = R_1 \parallel R_2$$

$$A_v \approx \frac{R_1 \parallel R_2}{R_G + R_1 \parallel R_2} \cdot \frac{-r_{o3}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$