

**EE105, Spring 1997
Midterm #2
Professor R. T. Howe**

(NOTE: Greek letters are sometimes written in Roman alphabet in all caps. Subscripts are written A_1, etc. Micro is sometimes represented by a 'u'.)

Default bipolar transistor parameters:

npn: $BETA_n = 100$, $V_{A_n} = 50V$, $V_{CE,sat} = 0.2V$.

pnp: $BETA_p = 50$, $V_{A_p} = 25V$, $V_{EC,sat} = 0.2V$.


Default MOS transistor parameters: note that LAMBDA depends on L!

NMOS: $MU_{nC_{ox}} = 50 \text{ uAV}^{-2}$, $LAMBDA_n = [0.1/L]V^{-1}$ (L in um) $V_{T_n} = 1V$.

PMOS: $MU_{pC_{ox}} = 25 \text{ uAV}^{-2}$, $LAMBDA_p = [0.1/L]V^{-1}$ (L in um) $V_{T_p} = -1V$.

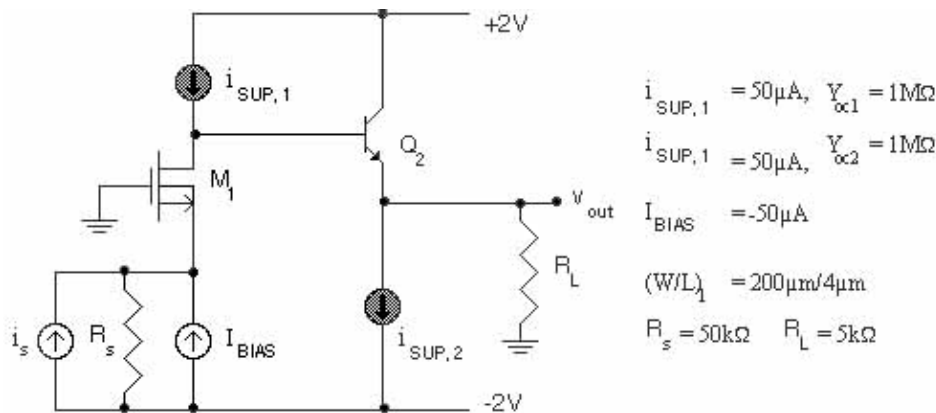Problem #1

BiCMOS Transresistance Amplifier [22 points]




- (a) [4 pts.] Draw the two-port small-signal model for this two-stage amplifier, with the small-signal source (and R_S) and the load resistor R_L attached. Your model should show the cascaded models for each stage; there is no need to substitute the expressions for the input and output resistances and gain elements for each stage.
- (b) [4 pts.] Find the numerical value of the input resistance of this amplifier, R_{in} .
- (c) [4 pts.] Find the numerical value of the output resistance of this amplifier, R_{out} . Your answer need only be correct to within plus or minus 5% for full credit.
- (d) [6 pts.] Find the numerical value of the transresistance R_m . Note that $R_S = \text{infinity}$ and $R_L = \text{infinity}$ for calculating this two-port parameter. Your answer need only be correct to within plus or minus 5% for full credit.
- (e) [4 pts.] If the current supplies I_{BIAS} , $i_{SUP,1}$, and $i_{SUP,2}$ all need a minimum voltage of 0.5 V across

them in order to function, what are the maximum and minimum values of v_{OUT} ? (In other words, find the output swing of the transresistance amplifier.)

Problem #2

Static CMOS Logic Gate [18 points]

 

(a) [5 pts.] What is the logic operation performed by the above circuit? In other words, what is the logical expression for Q in terms of the three inputs, A, B, and C? Note: you can use a truth table to answer this question.

(b) [4 pts.] We would like to have the worst case low-to-high and high-to-low propagation delays to be equal. Find the required relationship between the width-to-length ratio $(W/L)_n$ of the NMOS transistor and the width-to-length ratio $(W/L)_p$ of the PMOS transistors.

(c) [5 pts.] This logic gate has no load capacitance or wire capacitance (it does have parasitic drain-to-bulk capacitances, however.) Find the channel length transistors $L_p = L_n$ so that the worst case low-to-high propagation delay $t_{PLH} = 10^{-11}s = 100ps$.

Given: $\mu_{U_p} = 100 \text{ cm}^2/Vs$, $C_{ox} = 2.5 \text{ fF}/\mu\text{m}^2$, and the drain-to-bulk capacitance of each transistor is $C_{DB} = (1/3) C_{ox} W L$.

If you couldn't solve part (b), you can assume that $(W/L)_p = 2.5(W/L)_n$ for this part (not the correct answer to (b), of course.)


(d) [4 pts.] Find the ratio of the **best case** propagation delays.

$$t_{PHL}/t_{PLH}$$

If you couldn't solve (b), you can assume that $(W/L)_p = 2.5 (W/L)_n$ for this part (not the correct answer to (b), of course.)

Problem #3

Bipolar Transistor Physics [10 points]

 

Note: the default npn transistor parameters **do not apply to this problem!**

Given:

$$N_{dE} = 10^{18} \text{cm}^{-3},$$

$$N_{aB} = 5 \times 10^{16} \text{cm}^{-3},$$

$$N_{dC} = 4 \times 10^{15} \text{cm}^{-3}.$$

The base and emitter widths are $W_B = W_E = 0.25 \mu\text{m}$. The area of the emitter-base junction is $A_E = 1000 \mu\text{m}^2$ and the area of the base-collector junction is $A_C = 3000 \mu\text{m}^2$. The electron diffusion coefficient in the base is $D_{nB} = 10 \text{cm}^2/\text{s}$ and the hole diffusion coefficient in the emitter is $D_{pE} = 5 \text{cm}^2/\text{s}$. The charge on an electron is $q = 1.6 \times 10^{-19} \text{C}$.

- (a) [5 pts.] For the bias condition where $V_{OUT} = 2.5 \text{V}$, sketch the minority carrier concentration in the base on the graph below. Label the numerical value of $n_{pB}(x=0)$.
- (b) [5 pts.] Find the numerical value for the bias voltage V_{BIAS} for which the bipolar transistor just enters saturation ($V_{OUT} = 0.2 \text{V}$).

Solutions!

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**

**If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**