

Midterm #1 Solutions – EECS 145L Fall 2005

1a

$$V_0 = a V_+ + b V_-$$

$$V_0 = G_{\pm}(V_+ - V_-) + G_C(V_+ + V_-)/2$$

$$a V_+ + b V_- = (G_{\pm} + G_C/2) V_+ + (-G_{\pm} + G_C/2) V_-$$

$$a = G_{\pm} + G_C/2$$

$$b = -G_{\pm} + G_C/2$$

Adding, $G_C = a + b$

Subtracting, $G_{\pm} = (a - b)/2$

Alternative solution:

Since the common mode gain is the change in V_0 per unit change in $(V_+ + V_-)/2$, we can add 1 V to both V_+ and V_- and see that $\Delta V_0 = a + b$. So $G_C = a + b$

Since the differential gain is the change in V_0 per unit change in $(V_+ - V_-)$, we can add 0.5 V to V_+ , subtract 0.5 V from V_- and see that $\Delta V_0 = a/2 - b/2$. So $G_{\pm} = (a - b)/2$

2a

| | Op Amp | Inverting op-amp circuit amplifier | Non-inverting op-amp circuit amplifier | Differential op-amp circuit amplifier | Instrumentation amplifier |
|------------------------------------|--------|------------------------------------|----------------------------------------|---------------------------------------|---------------------------|
| High Z_{in} | YES | NO | YES | NO | YES |
| Differential input | YES | NO | NO | YES | YES |
| Defined gain over a frequency band | NO | YES | YES | YES | YES |

[1 point off for each wrong answer]

3a

At 10 Hz, $A = 10^5$ and the op-amp equation gives $V_3 = -V_0/10^5$ (virtual ground)

$$(V_1 - V_2)/100 \text{ k}\Omega - V_2/1 \text{ k}\Omega - V_2/1 \text{ k}\Omega = 0$$

$$V_1 - V_2 - 200V_2 = 0$$

$$\boxed{V_2 = V_1/201}$$

$$V_2/1 \text{ k}\Omega + V_0/100 \text{ k}\Omega = 0$$

$$100 V_2 + V_0 = 0$$

$$\boxed{V_0 = -100 V_2 \approx -0.5 V_1}$$

$$\boxed{V_3 = -0.5 \times 10^{-5} V_1 \text{ } (\approx 0 \text{ was also accepted)}}$$

3b

At 1 MHz, $A = 1$, the op-amp equation gives $V_0 = -V_3$

$$(V_1 - V_2)/100 \text{ k}\Omega + (V_3 - V_2)/1 \text{ k}\Omega - V_2/1 \text{ k}\Omega = 0$$

$$V_1 - V_2 + 100V_3 - 100V_2 - 100 V_2 = 0$$

$$V_1 + 100V_3 - 201V_2 = 0$$

Midterm #1 Solutions – EECS 145L Fall 2005

$$(V_2 - V_3)/1 \text{ k}\Omega + (V_0 - V_3)/100 \text{ k}\Omega = 0$$

$$100V_2 - 100V_3 + V_0 - V_3 = 0$$

$$100V_2 - 102V_3 = 0$$

$$V_2 \approx V_3$$

$$V_1 \approx 100V_3 \approx 100V_2 \approx -100 V_0$$

$$\boxed{V_3 \approx V_1/100}$$

$$\boxed{V_2 \approx V_1/100}$$

$$\boxed{V_0 \approx -V_1/100}$$

Alternative solution: solve for any value of A and plug in for 10 Hz and 10⁶ Hz

Op-amp equation $V_0 = -AV_3$

$$\text{Kirchhoff's current law at node } V_2: \frac{V_1 - V_2}{100 \text{ k}\Omega} + \frac{V_3 - V_2}{1 \text{ k}\Omega} + \frac{0 - V_2}{1 \text{ k}\Omega} = 0$$

$$V_1 = V_2 + 100V_2 - 100V_3 + 100V_2 = 201V_2 - 100V_3$$

$$\text{Kirchhoff's current law at node } V_3: \frac{V_2 - V_3}{1 \text{ k}\Omega} + \frac{V_0 - V_3}{100 \text{ k}\Omega} = 0$$

$$100V_2 = 100V_3 + V_3 - V_0 = (101 + A)V_3$$

$$V_1 = \left[\frac{201(101 + A)}{100} - 100 \right] V_3 = \left[\frac{10301 + 201A}{100} \right] V_3$$

$$V_1 = \left[201 - \frac{100(100)}{101 + A} \right] V_2 = \left[\frac{10301 + 201A}{101 + A} \right] V_2$$

$$\boxed{V_2 = \frac{(101 + A)V_1}{10301 + 201A} \approx \frac{1 + A/100}{100 + 2A} V_1}$$

$$\boxed{V_3 = \frac{100V_1}{10301 + 210A} \approx \frac{V_1}{100 + 2A}}$$

$$\boxed{V_0 = \frac{-100AV_1}{10301 + 201A} \approx \frac{-AV_1}{100 + 2A}}$$

f = 10 Hz, A = 10⁵

$$V_2 \approx V_1/201 \approx 5 \times 10^{-3} V_1$$

$$V_3 \approx 100V_1/(201 \times 10^5) \approx 5 \times 10^{-6} V_1$$

$$V_0 \approx -0.5 V_1$$

f = 1 MHz, A = 1


$$V_2 \approx 100V_1/10000 \approx 10^{-2} V_1$$

$$V_3 \approx 100V_1/10000 \approx 10^{-2} V_1$$

$$V_0 \approx -10^{-2} V_1$$


Midterm #1 Solutions – EECS 145L Fall 2005

4a

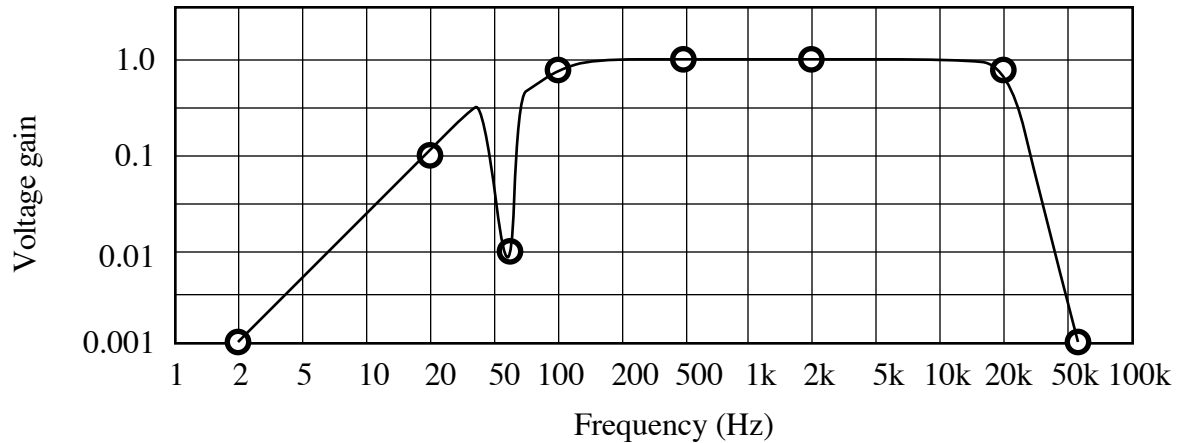

[1 point off for showing a constant gain of 0.001 below 2 Hz and above 55 kHz]

4b

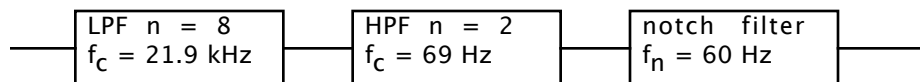

The LPF needs to have a gain $G_1 = 0.9$ at $f_1 = 20$ kHz and drop to a gain $G_2 < 0.001$ at $f_2 = 55$ kHz. Assuming that the corner frequency is near 20 kHz, find the smallest value of n for which the gain = 0.001 occurs at a value of f_2/f_c less than $55 \text{ kHz}/20 \text{ kHz} = 2.75$. Looking at the LPF table, we see that $f/f_c = 3.162$ at $n = 6$, $f/f_c = 2.371$ at $n = 8$, and $f/f_c = 1.995$ at $n = 10$.

Alternatively, we can use the fact that for a LPF with $G_2 \ll 1$, $G_2 \approx (f/f_c)^{-n}$ and $n = -\ln(G_2)/\ln(f/f_c) = -\ln(0.001)/\ln(55/20) = 6.83$.

Choosing $n = 8$, $G_1 = 0.9$ is at $f_1/f_c = 20 \text{ kHz}/f_c = 0.913$, and $f_c = 21,906$ Hz

$G_2 = 0.001$ is at $f_2/f_c = 2.371$ from which we compute $f_2 = 51,939$ Hz, which is less than 55 kHz as required.

LPF $n = 8$, $f_c = 21.91$ kHz

The HPF needs to have a gain $G_1 = 0.9$ at 100 Hz and drop to a gain $G_2 = 0.001$ at 2 Hz.

Assuming that the corner frequency is near 100 Hz, find the smallest value of n for which the gain = 0.001 occurs at a value of f_2/f_c greater than $2 \text{ Hz}/100 \text{ Hz} = 0.02$. Looking at the HPF table, we see that $f/f_c = 0.032$ at $n = 2$ and $f/f_c = 0.178$ at $n = 4$.

Alternatively, we can use the fact that for a HPF with $G_2 \ll 1$, $G_2 \approx (f/f_c)^n$ and $n = \ln(G_2)/\ln(f/f_c) = \ln(0.001)/\ln(2/100) = 1.77$.

Midterm #1 Solutions – EECS 145L Fall 2005

Choosing $n = 2$, $G_1 = 0.9$ is at $f_1/f_c = 100 \text{ Hz}/f_c = 1.437$, and $f_c = 69 \text{ Hz}$
 $G_2 = 0.001$ is at $f_2/f_c = 0.032$ from which we compute $f_2 = 2.2 \text{ Hz}$, which is greater than 2 Hz as required.

HPF $n = 2$, $f_c = 69 \text{ Hz}$

$n = 4$, $f_c = 83 \text{ Hz}$ was also accepted

The HPF has a gain just a bit below 0.7 at 60 Hz and does not meet the gain requirement of 0.01. A notch filter with accurate components should provide the necessary low gain.

[3 points off for using a 10 or 12 pole HPF rather than a notch filter to reduce the gain from 0.9 at 100 Hz to 0.01 at 60 Hz- this uses 4 or 5 more op-amps, is inefficient, and has more components that can fail]

145L midterm #1 grade distribution:

| | | | | |
|---------|-------------------------|-----------------|----------------|---|
| | | | | |
| | | maximum score = | 100 | |
| | | average score = | 91.4 (9.0 rms) | |
| Problem | | 65-69 | 0 | F |
| | | 70-74 | 1 | D |
| 1 | 13.0 (3.5 rms) (15 max) | 75-79 | 2 | C |
| 2 | 14.4 (1.2 rms) (15 max) | 80-84 | 1 | C |
| 3 | 32.3 (4.6 rms) (35 max) | 85-89 | 2 | B |
| 4 | 31.7 (5.0 rms) (35 max) | 90-94 | 3 | B |
| | | 95-99 | 5 | A |
| | | 100 | 5 | A |
| | | | GPA 3.26 | |