

NAME (please print) \_\_\_\_\_

STUDENT (SID) NUMBER \_\_\_\_\_

**UNIVERSITY OF CALIFORNIA, BERKELEY**

College of Engineering  
Electrical Engineering and Computer Sciences

**EECS 145M: Microcomputer Interfacing Lab**

LAB REPORTS:

1 _____	2 _____	3 _____
8 _____	9 _____	10 _____
21 _____	22 _____	23 _____
24 _____	26 _____	

Total of top 4 Long Lab Grades \_\_\_\_\_ (400 max)

Total of top 4 Short Lab Grades \_\_\_\_\_ (100 max)

Lab Participation \_\_\_\_\_ (100 max)

Mid-Term #1 \_\_\_\_\_ (100 max)

Mid-Term #2 \_\_\_\_\_ (100 max)

Final Exam \_\_\_\_\_ (200 max)

Total Course Grade \_\_\_\_\_ (1000 max)

COURSE LETTER  
GRADE

**Spring 2005 FINAL EXAM (May 14)**

Answer the questions on the following pages completely, but as concisely as possible. The exam is to be taken *closed book*. Use the reverse side of the exam sheets if you need more space. Calculators are OK.

*Partial credit can only be given if you show your work.*

**FINAL EXAM GRADE :**

1 \_\_\_\_\_ (40 max)      2 \_\_\_\_\_ (25 max)      3 \_\_\_\_\_ (25 max)

4 \_\_\_\_\_ (50 max)      5 \_\_\_\_\_ (60 max)

TOTAL \_\_\_\_\_ (200 max)

Initials \_\_\_\_\_

**PROBLEM 1** (total 40 points) Describe briefly how the following devices work (not just their definition):

**1a** (10 points) Digital to Analog converter (ladder or R-2R, your choice)

**1b** (10 points) Analog comparator

Initials \_\_\_\_\_

**1c** (10 points) Flash 8-bit A/D converter

**1d** (10 points) Half-flash 16-bit A/D converter

Initials \_\_\_\_\_

**PROBLEM 2** (total 25 points)

You have just tested an 8-bit D/A circuit by making measurements of its output glitches. You find that after a change in input at time  $t$ , the output glitch begins no earlier than  $t + 10$  ns and is gone after  $t + 30$  ns. The output ranges from  $V_1 = 0$  volts to  $V_{255} = 2.55$  volts.

**Design a circuit that eliminates glitches and has accurate conversion at 0 Hz.**

You have available the following components:

- A digital circuit that has 8 inputs and one output (normally low). If the input bits change at time  $t$ , the output goes high from  $(t + 5$  ns) to  $(t + 5$  ns +  $t_d$ ). You need to choose the value of  $t_d$ .
- A sample-and-hold amplifier with an analog input, and analog output, and a digital control line. When the control line is low, the analog output  $V_0(t)$  is equal to the analog input  $V_1(t)$ . When the control line is made high at time  $t_h$ , the analog output is initially held at  $V_1(t_h)$ , but has an output droop rate of 100 mV per second.

Do the following:

**2a** (15 points) Draw a block diagram of your circuit design, showing and labeling all essential components and connections.

Initials \_\_\_\_\_

**2b** (10 points) Briefly describe the operation of your circuit after a change in input.

**PROBLEM 3** (total 25 points)

You have a 16-bit successive approx A/D converter with  $10\ \mu\text{s}$  conversion time.

**3a** (10 points) What is the maximum frequency sinewave that changes less than  $1/2$  LSB during the conversion time?


**3b** (10 points) If you use a sample-and-hold amplifier, what is the time jitter requirement that would result in accurate sampling at the maximum conversion rate?

**3c** (5 points) Assuming the solution to 3b, what is the maximum frequency that can be accurately sampled (as limited by the Nyquist sampling theorem)?

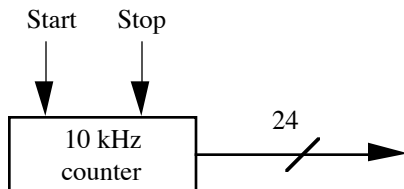**PROBLEM 4** (total 50 points):

Design a system for timing the swimming events in the Summer Olympic Games.

- There are 16 swimmers and the pool has 16 lanes. Each swimmer starts at the one end of the pool and, at the sound of a gunshot, jumps in and swims to the opposite end of the pool in their own lane
- When they reach the opposite end of the pool, the swimmers touch a plate mounted at the water line which briefly closes an electrical contact.
- The athletic event is started by an electronic starter's pistol, which makes a brief electrical contact when the trigger is pulled
- Your system detects the contact closure of the starter's pistol and immediately sends a pre-recorded gunshot sound to 16 speakers, each located behind a swimmer. (this gives each swimmer a fair start and also avoids using chemical explosives).
- There are 16 24-bit counter/timers, one for each lane. Each can be set to zero by the high-to-low edge of a "Start" input pulse, increases by one count every  $100 \mu s$ , and is stopped by the high-to-low edge of a "Stop" input pulse. The start and stop input lines float high when disconnected and can be brought low by connecting to ground.



- Your microcomputer has three 16-bit digital input ports, one 16-bit digital output port, and one analog output port.
- You have a power amplifier and 16 speakers
- You have 17 set/reset latches whose output state changes on a high-to-low edge of the inputs

The requirements for your design are:

- The system must record the time for every swimmer to an accuracy of  $100 \mu s$  even if several swimmers touch their plates in the same  $100 \mu s$ .
- The lane numbers and time for each swimmer (in units of s) are to be written to the computer display screen and to a file as soon as possible after the swimmer finishes.

Initials \_\_\_\_\_

- 4a** (25 points) Sketch your design, showing and labeling all essential components and lines. (You only need to show two touch plate switches, timing circuits and speakers.)

Initials \_\_\_\_\_

- 4b** (25 points) Describe the events (hardware and software) that must take place from the start of the race to when the last swimmer finishes and the results are displayed.



Initials \_\_\_\_\_

**PROBLEM 5** (total 60 points):

You have the following:

- a computer with an analog input/output port that can operate at a chosen rate up to  $10^6$  samples/s
- a loudspeaker that can convert an electrical waveform into an acoustic waveform. It has a frequency response that is above zero for frequencies between 20 Hz and 20 kHz, and essentially zero for frequencies below 10 Hz and above 40 kHz.
- a microphone that can accurately convert an acoustic waveform into an electrical waveform for frequencies between 10 Hz and 40 kHz.

**5a** (10 points) Design a system for determining the acoustic response of the speaker to an impulse electrical input. Sketch your design, showing and labeling all essential components and lines

**5b** (10 points) List the steps you would need to determine the acoustic response of the speaker to an impulse electrical input, sampled at 100 kHz.

Initials \_\_\_\_\_

**5c** (25 points) List the necessary steps for determining the digital filter  $b[i]$  so that if an analog electrical waveform  $a(t)$  is sampled at 100 kHz, filtered with  $b[i]$ , and the filter output is sent to the loudspeaker, then the acoustic waveform of the loudspeaker is a close representation of  $a(t)$  for frequencies between 20 Hz and 20 kHz.

**5d** (15 points) Sketch the block diagram of a system that implements the procedure of part 5c. Show and label all essential components and lines.