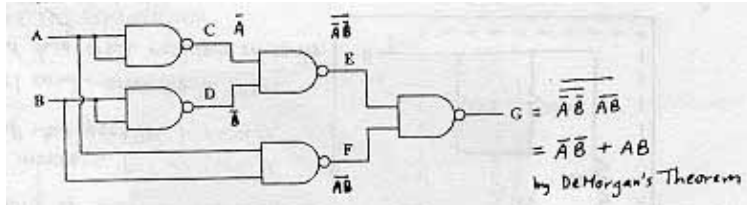


**EECS40, Spring 2000
Midterm 1 solutions
Prof King**

Problem #1



a)

A	B	G
0	0	1
0	1	0
1	0	0
1	1	1

b)


$$G = (\text{not } A)(\text{not } B) + AB$$

c)

3 unit gate delays

The longest path between the input variables and the output variable is 3 logic gates. Therefore, we need to wait for a period of 3 unit gate delays after an input variable is changed, before we can trust the value of G to be valid.


d)

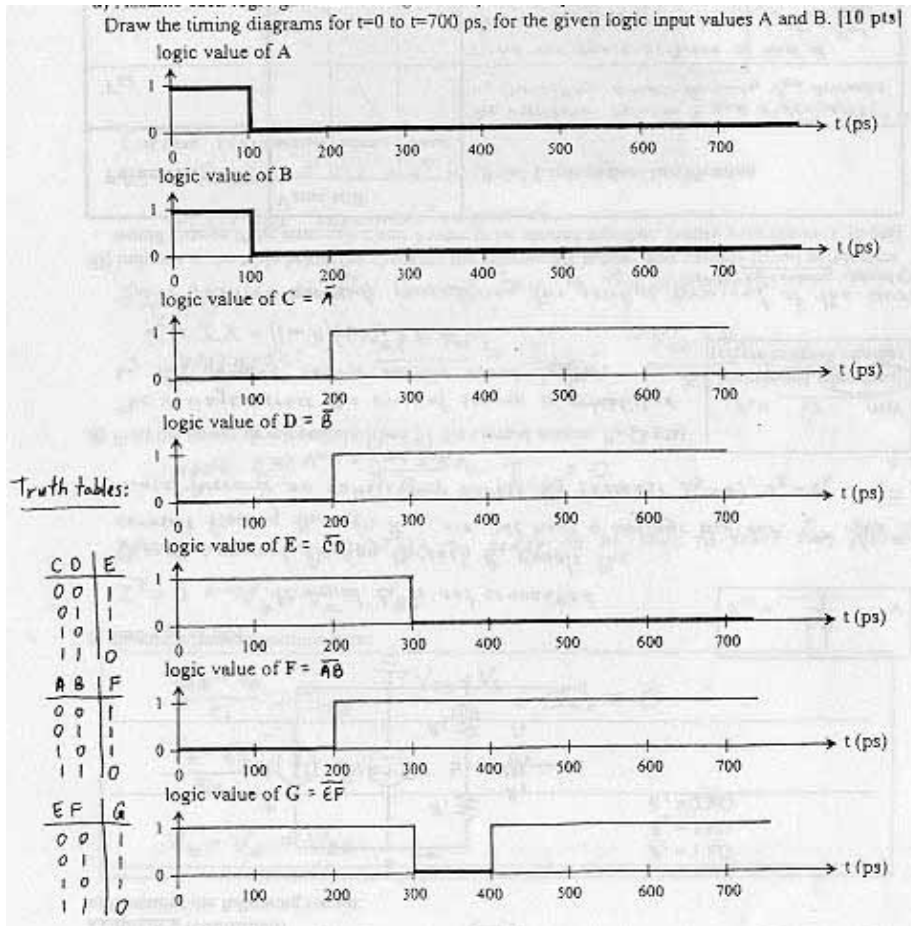


Problem #2

a)

$R_{ab} = 13$ ohms

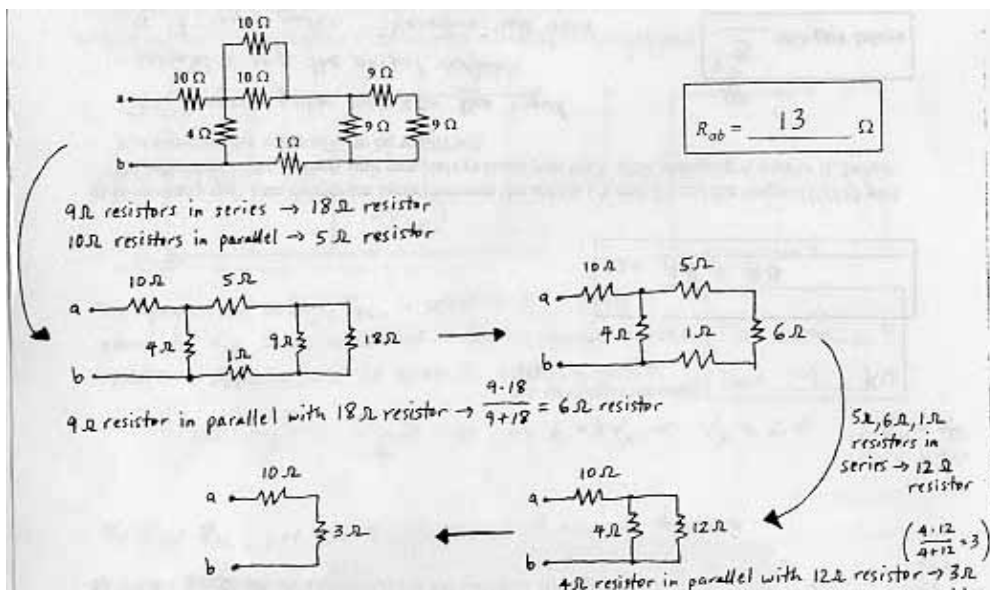

b)

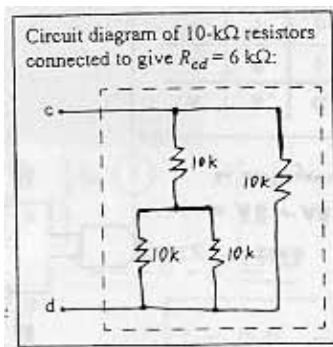

- * To achieve an equivalent resistance lower than the individual resistors, we should connect resistors in parallel
- * But the parallel combination of 2 10 kohm resistors is 5 kohm -- too low!
- => need to increase the resistance of one of the parallel branches
- * Try parallel combination of a 10 kohm resistor and 2 10 kohm resistors in series:
 $(20 \cdot 10) / (20 + 10) = 6.7 \text{ kohm}$ -- too high!
- * Try increasing the resistance of one parallel branch by only 5 kohm (10 kohm || 10 kohm) instead of 10 kohm
 $(15 \cdot 10) / (15 + 10) = 6 \text{ kohm}$!

c)

(ground is placed at the bottom of the diagram)

i)

$V_{cd} = 4 \text{ V}$

$I_3 = 0$ since terminal c is not connected. Thus the current flowing through R1 equals the current flowing through R2, i.e. we have a voltage divider.
 $\Rightarrow V_{bd} = (R_2 / (R_1 + R_2)) \cdot 6 = (2 / (1 + 2)) \cdot 6 = 4 \text{ V}$
 Since there is no voltage drop across R3 (because $I_3 = 0$), $V_c = V_b$
 $\Rightarrow V_{cd} = V_{bd} = 4 \text{ V}$

ii)

(underscore denotes subscript for uppercase variables)

$P_I = 6 \text{ mW}$ absorbed

The voltage across the current source is established by the voltage source and is equal to 6 V.
 $P_I = IV = (1 \text{ mA})(6 \text{ V}) = 6 \text{ mW}$
 Since positive current is entering the positive terminal of the current source it is absorbing power

iii)

Parameter	value will:	Brief Explanation
V_{bd}	decrease	The resistance between b and d decreases; by the voltage-divider formula, V_{bd} decreases

b)

I1	increase	Total resistance between a and d decreases; Vad remains 6V; I1 = Vad/Rad
Power developed by voltage source	increase	Since I1 increases, the current supplied by the voltage source increases

iv)

I3 = 1.5 mA

Equivalent resistance between terminals a and d is

$$R1 + R2 || R3 = 1 + (2*2)/(2+2) = 2 \text{ kohm}$$

$$\Rightarrow I1 = (6 \text{ V})/(2 \text{ kohm}) = 3 \text{ mA}$$

$$\text{Using current-divider formula, } I3 = (2/(2+2))*(3 \text{ mA}) = 1.5 \text{ mA}$$

Problem #3

(underscore denotes subscript for uppercase variables)

a)

nodal equations:

$$(V_{AA} - Va)/R1 + I_{BB} - I_{CC} + (Vb - Va)/R3 = 0$$

$$(Va - Vb)/R3 - (V_{BB} + Vb)/R4 + (Vc - Vb)/R5 = 0$$

$$I_{CC} + (Vb - Vc)/R5 - Vc/R6 = 0$$

Apply Kirchhoff's Current Law to nodes a, b, c:

(sum of currents entering a node = 0)

get 3 independent equations for 3 unknowns (Va, Vb, Vc) => can solve to find unknowns


b)

nodal equations:

$$(V_{AA} - Va)/R1 + I_{BB} - (V_{CC} + Vb)/R3 + I_{CC} = 0$$

$$(Vb - Vc)/R4 + I_{CC} = 0$$

$$Vb - Va = V_{BB}$$

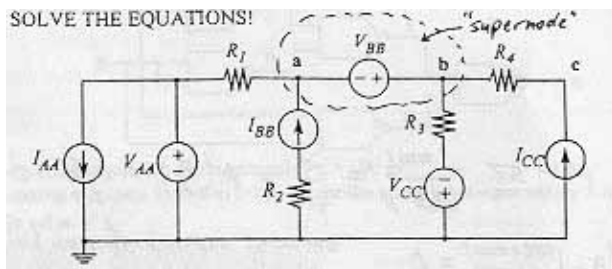

Current flowing through the voltage source V_BB cannot be expressed as a function of the node voltages Va and Vb

=> use the "supernode" approach

Applying Kirchhoff's Current Law to the supernode and node c:

$$\text{supernode: } (V_{AA} - Va)/R1 + I_{BB} + (-V_{CC} - Vb)/R3 + I_{CC} = 0$$

$$\text{node c: } (Vb - Vc)/R4 + I_{CC} = 0$$

Need one more equation in order to be able to solve for the 3 unknowns:

$$Vb - Va = V_{BB}$$

iii)

Problem #4

a)

$V_{Th} = 2\text{ V}$
 $R_{Th} = 4\text{ kohm}$


(x is the node between the 3 kohm and 2 kohm resistors)

The open-circuit voltage, V_{oc} , is equal to V_{ab} , which is equal to V_{xb} since no current is flowing through the 2 kohm resistor. Applying KCL to node x (defining node b as the reference node)

$\rightarrow (5 - V_x)/3 + (-4 - V_x)/6 = 0$

$\Rightarrow 6 = 3 V_x \Rightarrow V_x = 2\text{ V}$ therefore $V_{oc} = V_{Th} = 2\text{ V}$

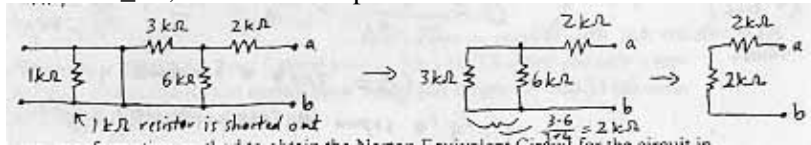To find R_{Th} , set all the independent sources to zero:




b)

$I_N = 0.5\text{ mA}$
 $R_N = 4\text{ kohm}$

$R_N = R_{Th} = 4\text{ kohm}$

$I_N = V_{Th}/R_{Th} = (2\text{ V})/(4\text{ kohm}) = 0.5\text{ mA}$

c)

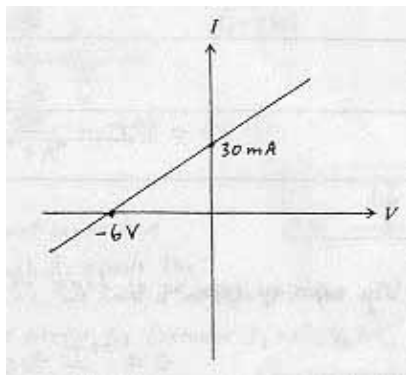


When $I = 0$, $V = -6\text{ V}$

When $V = 0$ (i.e. terminals a and b shorted together), $I = (0 - (-6\text{ V}))/200 \Rightarrow I = 30\text{ mA}$

d)

$P_{1k} = 25\text{ mW}$

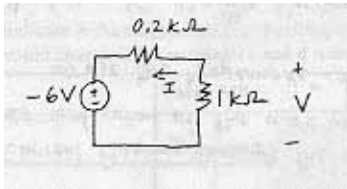nodal equations: $(V_{AA} - V_a)/R_1 + I_{BB} - (V_{CC} + V_b)/R_3 + I_{CC} = 0$
 $(V_b - V_c)/R_4 + I_{CC} = 0$
 $V_b - V_a = V_{BB}$



Using voltage-divider formula,

$$V = (1000/(1000+200))*(-6) = -5 \text{ V}$$

$$P = IV = (V/R)*V = V^2/R = ((-5)^2)/1000 = 25 \text{ mW}$$

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley
If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**