

EE 40/42/100, Spring 2007
Prof. Chang-Hasnain
Midterm #2

April 11, 2007

Total Time Allotted: 80 minutes

Total Points: 100

1. This is a closed book exam. However, you are allowed to bring two page (8.5" x 11"), single-sided notes.
2. No electronic devices, i.e. calculators, cell phones, computers, etc.
3. SHOW all the steps on the exam.
4. **Remember to put down units.** Points will be taken off for answers without units.

Last (Family) Name: _____

First Name: _____

Student ID: _____ Signature: _____

Circle the class you are in:


EE 40	EE 42	EE 100
-------	-------	--------

Circle one discussion session you are in

	Monday		Tuesday		Wednesday		Thursday		Friday	
	Dis	TA	Dis	TA	Dis	TA	Dis	TA	Dis	TA
10:00	100(42)-101	Richard					40-105	Mike	100-107	Haibo
11:00	40-101	Mike	100-105	Haibo	100(42)-102	Tanya				
13:00	40-102	Jia	40-103	Isaac	100-104	Tanya				
15:00			100-106	Haibo						

Problem 1 (22 pts)	
Problem 2 (10 pts):	
Problem 3 (15 pts)	
Problem 4 (18 pts)	
Problem 5 (35 pts):	
Total	

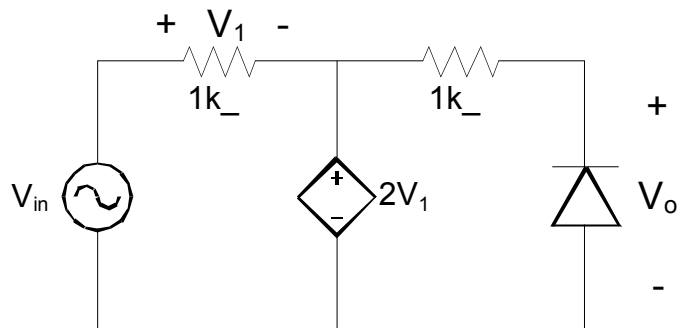1. (22 pts) Assume the diode in the circuit below using the **simple piecewise model with a threshold voltage of 0.6V** (also known as the **large signal model** in the text book).



(i) (4 pts) Re-draw the circuit assuming the diode is off. Express V_o as a function of V_{in} .

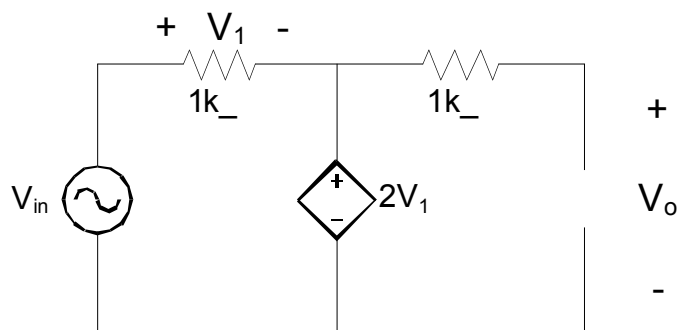


Figure 1 pt

$V_{in} = V_1 + 2V_1$ (1pts)

$V_1 = V_{in}/3$ (1pts)

$V_0 = 2V_1 = 2V_{in}/3$ (1pts)

(ii) (4 pts) Re-draw the circuit assuming the diode is on. Express V_o as a function of V_{in} .

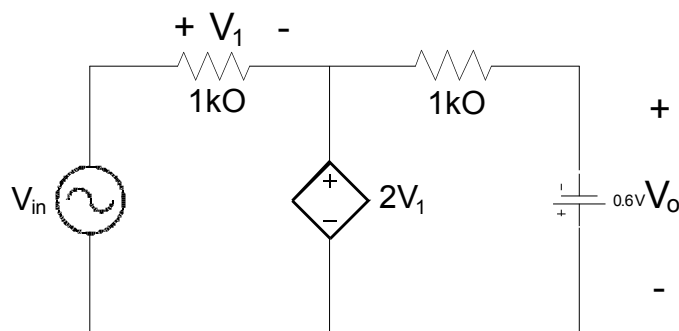


Figure 1 pt


$V_0 = -0.6 V$ (3 pts)

(iii) (4 pts) For what values of V_{in} will the diode be on?

$2V_{in}/3 \leq -0.6V$ (2pts)

$V_{in} \leq -0.9V$ (2pts)


(iv) (4 pts) Plot V_o vs. V_{in} .

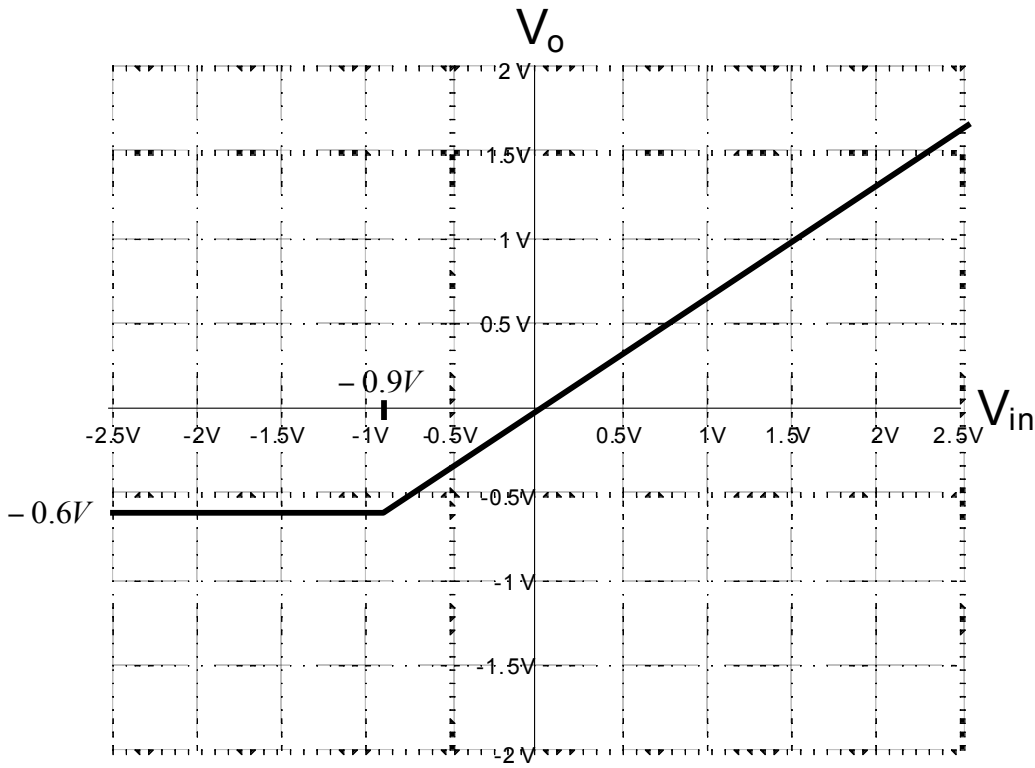

-0.9V, -0.6V,

positive side slope and shape (each 1pts)

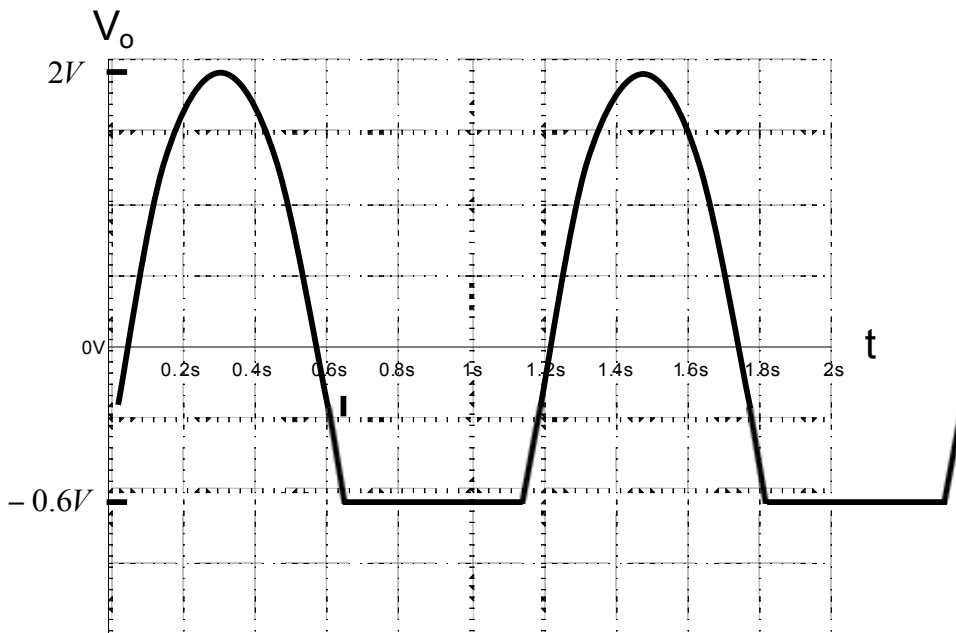(v) (6 pts) Now suppose $V_{in} = 3 \sin(2\pi t)$. Plot V_o versus time for $0 < t < 2s$. Label important voltages.




$$V_o = -0.6V = 3 \sin(2\pi t)$$

$$t = \frac{\sin^{-1}(-0.3)}{2\pi}$$

2V, -0.6V, clamping on reverse side each are 2 pts.

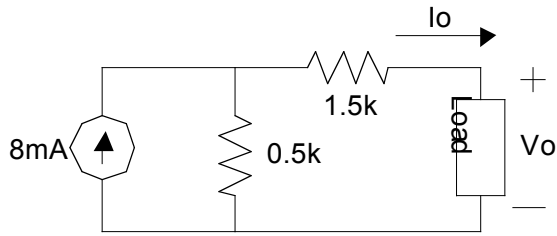2 (10 pts) Consider the following circuit:




(i) (4 pts) Derive an expression relating I_o to V_o .

$$(8\text{mA} - I_o) \cdot 0.5\text{k} = I_o \cdot 1.5\text{k} + V_o$$

$$4 = 2\text{k} \cdot I_o + V_o$$

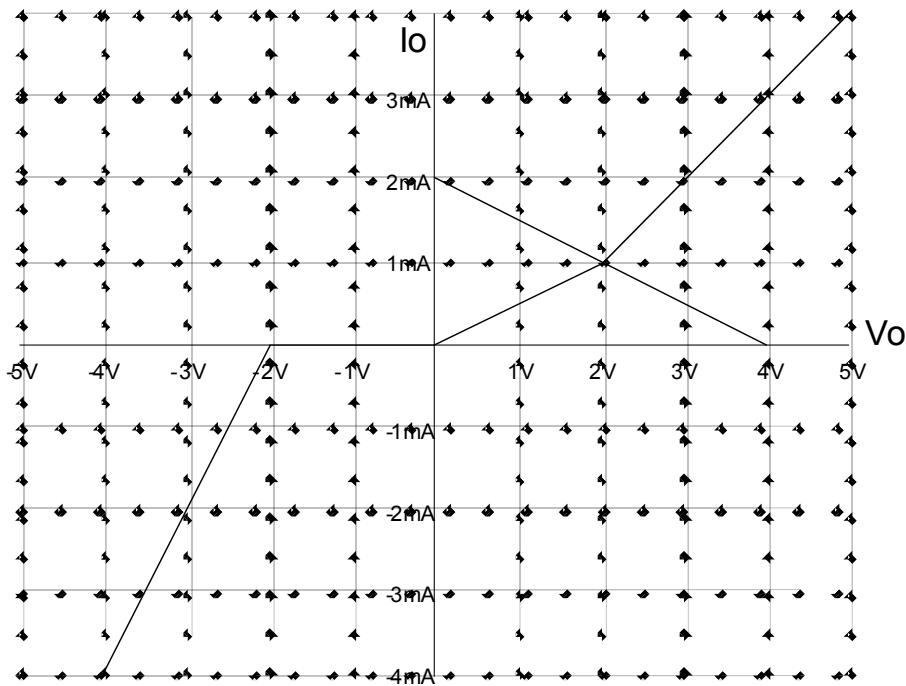(ii) (6 pts) Now assume the load has the following I-V characteristic. Draw a **load line** and find the values of I_o and V_o .




$$I_o = 1\text{mA}$$

$$V_o = 2\text{V}$$

3. (15 pts) Op-amp circuit:

For the figure below:

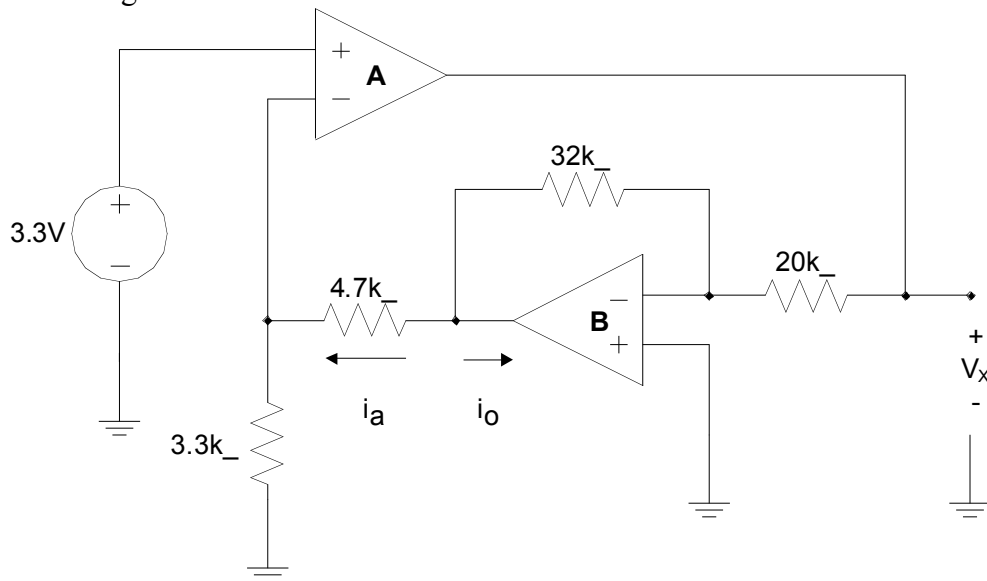

Assume both are ideal op-amps:

1. Find i_a .

$$i_a = 3.3\text{V}/3.3\text{K} = 1\text{mA}$$


2. Find i_o .

$$i_o = -(3.3\text{V} + 4.7\text{K} \cdot 1\text{mA})/32\text{K} - i_a = -1.25\text{mA}$$

3. Find V_x .

$$V_x = -0.25\text{mA} \cdot 20\text{K} = -5\text{V}$$

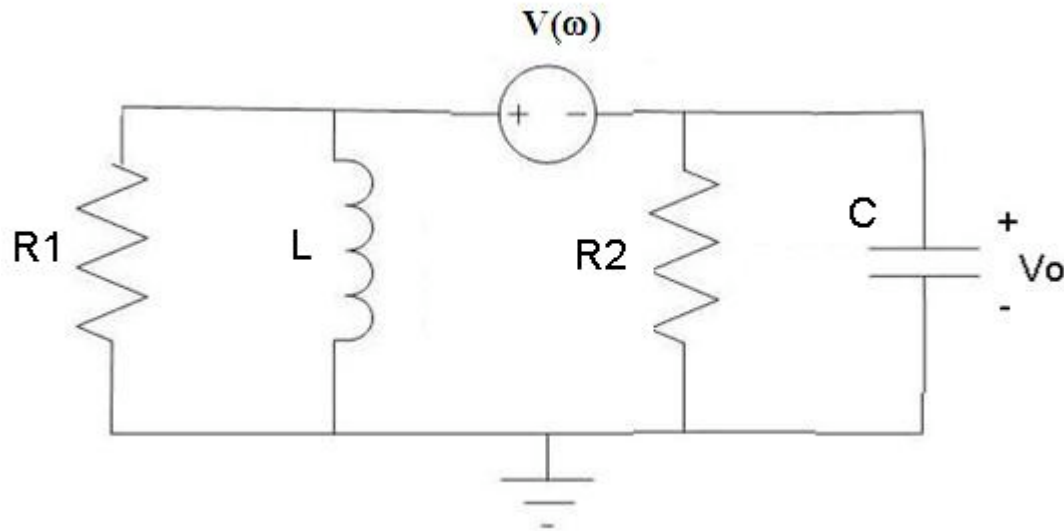4. (18 pts) Consider the following circuit: Find the transfer function $V_o/V_{in}(\omega)$



There are many different ways to solve this problem. I think voltage divider and KCL are the simplest.

Voltage divider method:

$$\frac{V_o}{V_{in}} = \frac{R_2 \parallel \frac{1}{j\omega C}}{R_1 \parallel (j\omega L) + R_2 \parallel \frac{1}{j\omega C}} = \frac{\frac{R_2}{1 + j\omega R_2 C}}{\frac{j\omega R_1 L}{R_1 + j\omega L} + \frac{R_2}{1 + j\omega R_2 C}}$$

You **DON'T** have to simplify that to get full credit. However, in case you do simplify it, you should be able to get something similar to the following:

$$\begin{aligned} \frac{V_o}{V_{in}} &= \frac{\frac{R_2}{1 + j\omega R_2 C}}{\frac{j\omega R_1 L * (1 + j\omega R_2 C) + R_2 * (R_1 + j\omega L)}{(1 + j\omega R_2 C) * (R_1 + j\omega L)}} = \frac{R_2 * (R_1 + j\omega L)}{j\omega R_1 L * (1 + j\omega R_2 C) + R_2 * (R_1 + j\omega L)} \\ &= \frac{R_1 R_2 + j\omega R_2 L}{R_1 R_2 - \omega^2 R_1 R_2 C L + j\omega L (R_1 + R_2)} \end{aligned}$$

KCL @ ground method:

$$\frac{V_1}{R_1} + \frac{V_1}{j\omega L} + \frac{V_o}{R_2} + V_o j\omega C = 0 \quad \text{where } V_1 = V_o + V_{in}$$

$$\frac{V_o + V_{in}}{R_1} + \frac{V_o + V_{in}}{j\omega L} + \frac{V_o}{R_2} + V_o j\omega C = 0$$

$$\frac{V_o}{V_{in}} = - \frac{\frac{1}{R_1} + \frac{1}{j\omega L}}{\frac{1}{R_1} + \frac{1}{j\omega L} + \frac{1}{R_2} + j\omega C}$$

It can be further simplified to the result in voltage divider.

5. (35 pts) Consider the following transfer function of a circuit.

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{a}{1 + jf / f_B} \quad \text{Let } a = 10, f_B = 1 \text{ kHz.}$$

(a) (5 pts) Write an expression for $|H(f)|$ in dB.

$$|H(f)| = 10 / \sqrt{1 + (f/f_B)^2}$$

$$20 \lg |H(f)| = 20 - 10 \lg(1 + (f/f_B)^2)$$

(b) (4 pts) Evaluate (approximate) this expression for $f \ll f_B$. Find $|H(f)|$ and the slope in the region.

$$|H(f)| = 20 \log a = 20$$

Slope: 0dB/decade

(c) (3 pts) Evaluate (approximate) this expression for $f \gg f_B$. What is the slope?

$$20 - 20 \log(f / f_B)$$

Slope: -20dB/decade

(d) (2 pts) Evaluate this expression for $f = f_B$ (What is $|H(f_B)|_{dB}$ exactly?).

$$20 - 10 \log 2$$

(e) (5 pts) Write an expression for $\angle H(f)$.

$$- \arctan (f/f_B)$$

(f) (3 pts) Evaluate this expression for $f \ll f_B$. Find $\angle H(f)$.

$$0^\circ$$

(g) (3 pts) Evaluate this expression for $f \gg f_B$. Find $\angle H(f)$.

$$-90^\circ$$

(h) (3 pts) Evaluate this expression for $f = f_B$. Find $\angle H(f_B)$.

(i) (2 pts) What type of filter is this?

Low pass filter

(j) (5 pts) Suppose the input signal is given by:

$$v_{in}(t) = 5 + 10 \cos(10^3 * 2\pi * t) + 10 \cos(10^4 * 2\pi * t - 50^\circ)$$

Find an expression for the output $v_{out}(t)$

(Hint: $\frac{1}{\sqrt{1.01}} \approx 0.995$, $\frac{1}{\sqrt{2}} \approx 0.7071$, $\frac{1}{\sqrt{101}} \approx 0.0995$,

$\arctan 0.1 \approx 5.71^\circ$, $\arctan 10 \approx 84.29^\circ$) These may not all be needed.

$$\begin{array}{lll} 5 & \rightarrow & 50 \\ 10\cos(10^3*2\pi*t) & \rightarrow & 100 * 0.7071\cos(10^3*2\pi*t -45^\circ) \\ 10\cos(10^4*2\pi*t-50^\circ) & \rightarrow & 100 * 0.0995\cos(10^4*2\pi*t -50^\circ-84.29^\circ) \end{array}$$

$$V_{out}(t) = 50 + 100 * 0.7071\cos(10^3*2\pi*t -45^\circ) + 100 * 0.0995\cos(10^4*2\pi*t -50^\circ-84.29^\circ)$$