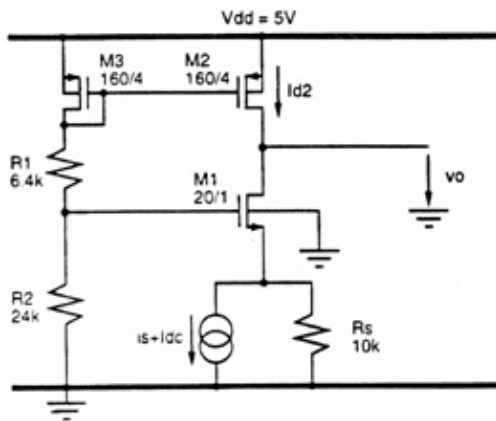


**EE 140, Spring 1995
Midterm 1
Prof. Boser**

Problem #1

In the amplifier shown below the dc bias I_{dc} is adjusted such that all devices operate in the forward active region.


- (a) Find I_{d2} , the drain current in M2.
- (b) Find the transresistance $R_x = v_o/i_s$. Don't neglect the body effect and beware that λ depends on channel length.
- (c) What are the minimum and maximum output voltages that keep all devices in saturation?



Problem #2

Assume that the all npn reference shown below has a stable operating point without startup problem and that all devices are in the forward active region. Neglect base currents and device output impedance.

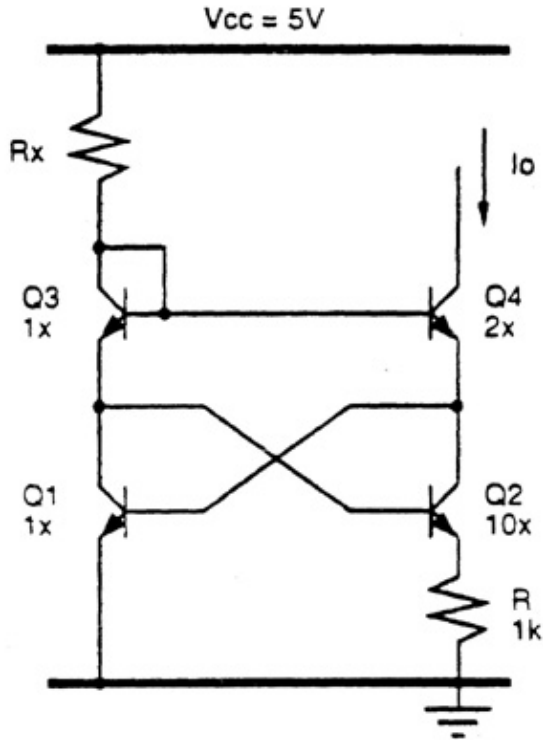
- (a) Find I_o at 300K.
- Hint: find a loop around which all voltages sum to zero.
- (b) Find the value of the fractional temperature coefficient(TCF) of I_o .
- (c) What type of reference is this? (e.g. band-gap, V_t -referenced, etc).
- (d) What is the minimum voltage required at the output to keep Q4 forward active?



Problem #3

Shown below is a simplified schematic of the input stage of an operational amplifier. Notice that Q1 and Q2 are not an emitter coupled pair.

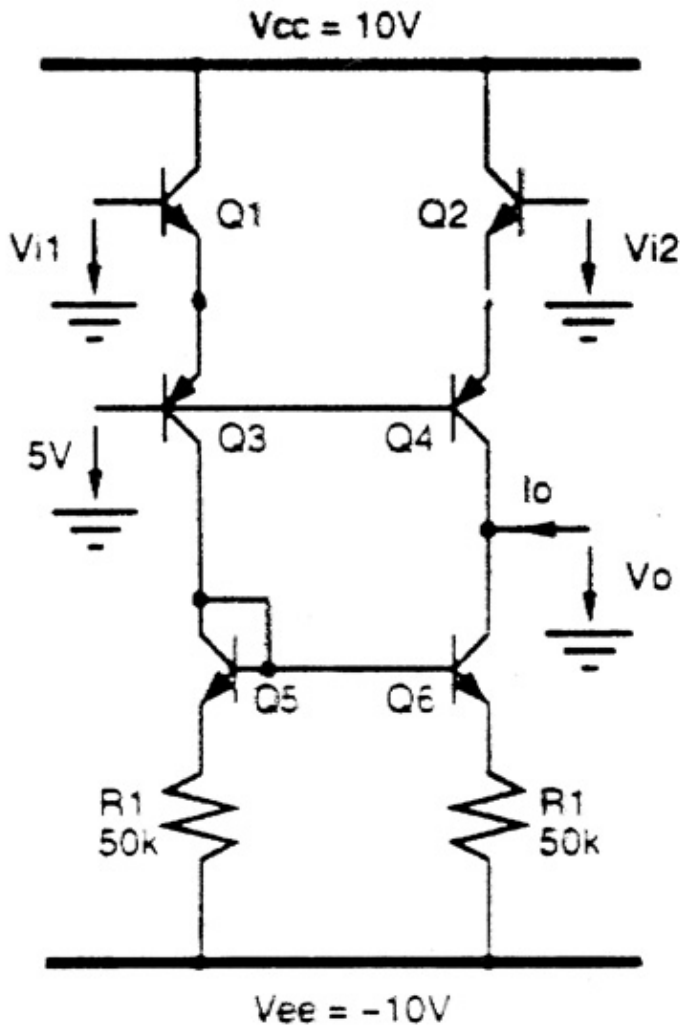- (a) Find the input common-mode voltage $v_{ic} = (v_{i1} + v_{i2})/2$ for which $I_{c1} = I_{c2} = 10$ microAmps. For this condition (i.e. $I_{c1} = I_{c2} = 10$ microAmps),
- (b) Find the differential transconductance $G_m = i_0/v_{id}$ ($v_{id} = v_{i1} - v_{i2}$), output impedance $R_o = v_o / i_o$, and the differential voltage gain v_o/v_{id} of the circuit.
- (c) What are the minimum and maximum values of V_o for which all devices remain in the forward active region?



Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley
If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.