



University of California  
 College of Engineering  
 Department of Electrical Engineering  
 and Computer Sciences

E. Alon

Tuesday, October 6, 2009  
 6:30-8:00pm

## EECS 141: FALL 2009—MIDTERM 1

For all problems, you can assume that all transistors have a channel length of 90nm and the following parameters (unless otherwise mentioned):

**NMOS:**

$$V_{Tn} = 0.2V, \mu_n = 400 \text{ cm}^2/(V \cdot s), C_{ox} = 1.125 \text{ } \mu\text{F}/\text{cm}^2, v_{sat} = 1e7 \text{ cm/s}, \lambda = 0$$

**PMOS:**

$$|V_{Tp}| = 0.2V, \mu_p = 200 \text{ cm}^2/(V \cdot s), C_{ox} = 1.125 \text{ } \mu\text{F}/\text{cm}^2, v_{sat} = 1e7 \text{ cm/s}, \lambda = 0$$

<b>NAME</b>	Last <i>Solutions</i> First
-------------	-----------------------------

<b>GRAD/UNDERGRAD</b>	
-----------------------	--


**Problem 1:** \_\_\_\_ / 30

**Problem 2:** \_\_\_\_ / 20

**Problem 3:** \_\_\_\_ / 20

**Total:** \_\_\_\_ / 70

 **PROBLEM 1. Logical Effort and Gate Sizing (30 points)**



a) (6 pts) What is the path effort from In to Out?

$$F = 300\text{fF} / 5\text{fF} = 60$$

$$\pi LE = 2 \cdot 5 / 3 = 10/3$$

$$\pi B = 2$$

$$PE = F \cdot \pi LE \cdot \pi B$$

$$\boxed{PE = 400}$$

b) (2 pts) What EF/stage minimizes the delay of this chain of gates?

$$EF_{opt} = \sqrt[5]{PE}$$

$$\boxed{EF_{opt} \approx 3.31}$$

c) (8 pts) Size the gates to minimize the delay from In to Out.

$$d = \frac{300\text{fF}}{3.31} \approx 90.63\text{fF}$$

$$c = \frac{d}{3.31} \approx 27.38\text{fF}$$


$$b = \frac{5}{3} \cdot \frac{c}{3.31} \approx 13.79\text{fF}$$

$$a = 2 \cdot \frac{b}{3.31} \approx 8.33\text{fF}$$

Size	Value (fF)
a	8.33
b	13.79
c	27.38
d	90.63

- d) (6 pts) While maintaining the same logical functionality and without changing  $C_{in}$ , can you improve the delay of this chain of gates (repeated below) by changing the number and/or types of gates? Please draw an improved schematic for the new chain of gates; you don't need to provide gate sizes.


Original chain:

 

Improved chain:

Optimal number of stages:  $\log_4(400) \approx 4.32$

 So, 5 stages is about right. However, we have a 4-input NAND (which has large LE) at the beginning of the chain, and we also have a bunch of inverters. So, in order to reduce the LE, we can replace the 4-input gate with a cascade of 2-input gates and inverters:



- e) (8 pts) Now let's imagine that you are working in a new technology where the  $\gamma$  ( $= C_D/C_G$ ) of the transistors is 100. Now how would you redesign the chain of gates in order to improve its delay? Please draw an improved schematic for the new chain of gates; you don't need to provide gate sizes. (You will receive partial credit if you can explain in general how  $\gamma$  should affect the design of the chain.)

Remember that delay optimal  $f$  (and equivalently,  $EF$ ) is set only by  $\gamma$ :


$$f = e^{(1+\gamma/f)}$$

$$\gamma = 100 \rightarrow f \approx 37.9$$

In other words, with such a large  $\gamma$ , the optimal fanout is also substantially larger than 4. Therefore, the optimal number of stages will be much smaller:


$$N_{opt} = \log_{37.9}(PE) \approx 1.65$$

To get the logical polarity right, this would lead us to a 1 stage implementation.

 


**PROBLEM 2. (20 pts) Complex Gates and Delay.**

 - a) (4 pts) Implement the function  $F = \overline{((A \cdot B) + C)} \cdot D$  with a complex static CMOS gate.



 - b) (4 pts) Assuming  $R_{sqp} = R_{sqn}$ , size your gate so that the worst-case pull up resistance is equal to the worst-case pull-down resistance. What is the logical effort of this gate from the A input?




$$LE_A = \frac{C_{inA}}{C_{in,inv}}$$

$$LE_A = \frac{5}{2}$$



 
c) (12 pts) Using the switch model for the transistors, what is the worst-case delay of the gate shown below? You can assume that  $C_G = C_D = 2\text{fF}/\mu\text{m}$ ,  $R_{\text{sqn}} = 10\text{k}\Omega/\square$ , and  $R_{\text{sqp}} = 20\text{k}\Omega/\square$ , and you should provide your answer in ps.



The first thing to realize here is that the worst-case delay occurs when  $A=B=1$  and  $C$  goes from 1 to 0.

(You can see this by noticing that in this case a single PMOS transistor has to drive all of the internal caps of the stack.)

RC model:

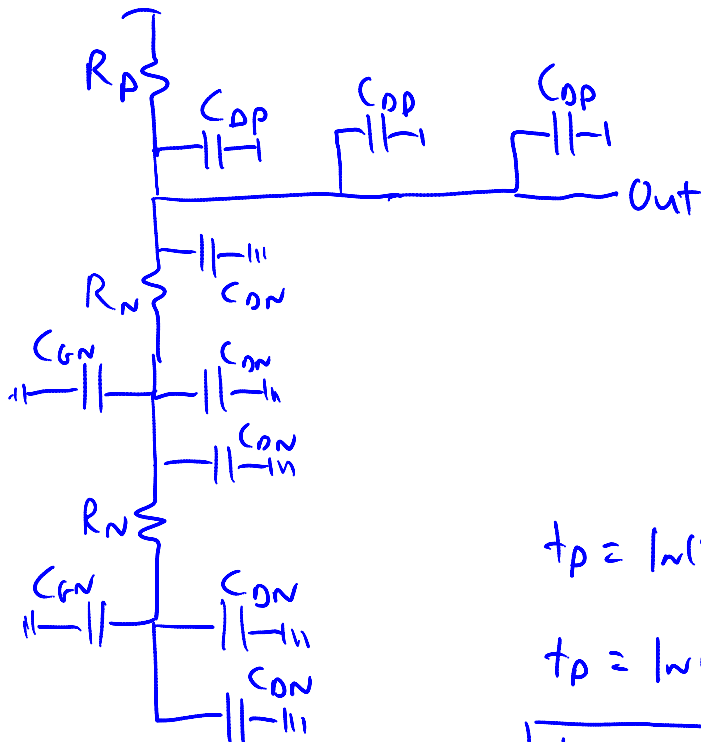

$$R_p = 20\text{k}\Omega/\square \cdot \frac{90\text{nm}}{1\mu\text{m}} = 1.8\text{k}\Omega$$

$$R_n = 10\text{k}\Omega/\square \cdot \frac{90\text{nm}}{1.5\mu\text{m}} = 600\Omega$$

$$C_{dp} = 2\text{fF}/\mu\text{m} \cdot 1\mu\text{m} = 2\text{fF}$$

$$C_{dn} = 2\text{fF}/\mu\text{m} \cdot 1.5\mu\text{m} = 3\text{fF}$$

$$C_{gn} = C_{gn} = 3\text{fF}$$


$$t_p \approx \ln(2) \cdot R_p \cdot (3C_{dp} + 5C_{dn} + 2C_{gn})$$

$$t_p \approx \ln(2) \cdot 1.8\text{k}\Omega \cdot (6\text{fF} + 15\text{fF} + 6\text{fF})$$


$$t_p \approx 33.7\text{ps}$$

**PROBLEM 3. (20 pts) Miscellaneous**


- a) (8 pts) Using the simple switch model of the transistors with  $R_{sqn} = 10k\Omega/\square$ ,  $R_{sqp} = 20k\Omega/\square$ , and  $V_{TN} = |V_{TP}| = 0.2V$ , draw the VTC of the circuit shown below and provide the values of  $V_{OH}$ ,  $V_{OL}$ ,  $V_{IH}$ , and  $V_{IL}$ . You can assume that the NMOS and PMOS transistors inside of the inverters are sized such that their on-resistances are equal.

 


VTC of P:

 

VTC of N:

 

VTC from  $I_n$  to  $O_{ut}$

 


$$V_{OH} = 1.2V$$

$$V_{OL} = 0V$$

$$V_{IH} = 0.8V$$

$$V_{IL} = 0.8V$$

 - b) (6 pts) Using the velocity saturated model and assuming that both of the transistors below operate in saturation, what value of  $V_{in}$  makes the drain current of the two transistors equal to each other?



$$\xi_{cn} = \frac{2v_{sat}}{\mu_n} = \frac{2e7 \text{ cm/s}}{400 \text{ cm}^2/\text{Vs}} = 5 \text{ MV/m}$$

$$\xi_{cp} = \frac{2v_{sat}}{\mu_p} = \frac{2e7 \text{ cm/s}}{200 \text{ cm}^2/\text{Vs}} = 10 \text{ MV/m}$$

$$I_{Dp} = W_p v_{sat,p} C_{ox,p} \frac{(1.2\text{V} - V_{in} - |V_{Tp}|)^2}{1.2\text{V} - V_{in} - |V_{Tp}| + \xi_{cp} \cdot L} \quad \xi_{cp} L = 0.9\text{V}$$

$$I_{Dn} = W_n v_{sat,n} C_{ox,n} \frac{(1\text{V} - V_{Tn})^2}{1\text{V} - V_{Tn} + \xi_{cn} L} \quad \xi_{cn} L = 0.45\text{V}$$

$$I_{Dp} = I_{Dn} \rightarrow I_{Dp}/I_{Dn} = 1$$


$$\frac{I_{Dp}}{I_{Dn}} = \frac{2\mu\text{m}}{1\mu\text{m}} \cdot \frac{(1\text{V} - V_{in})^2 // (1\text{V} - V_{in} + 0.9\text{V})}{(0.8\text{V})^2 / (0.8\text{V} + 0.45\text{V})} = 1$$

$$(1\text{V} - V_{in})^2 = 0.256\text{V} \cdot (1.9\text{V} - V_{in})$$


$$\rightarrow \boxed{V_{in} \approx 375 \text{ mV}}$$



 - c) (6 points) How much total energy is dissipated by the inverter shown below when  $I_n$  steps from 1.2V to 0V and then back to 1.2V? You can ignore all capacitors associated with the transistors inside of the inverter.




$I_n: 1.2V \rightarrow 0V:$

 

$$Q = (1.2V - 0.6V) \cdot 50fF = 30fC$$

$$E_{1.2V} = Q \cdot 1.2V = 36fJ$$

$I_n: 0V \rightarrow 1.2V:$

 

$$Q = (0.6V - 1.2V) \cdot 50fF = -30fC$$

$$E_{0.6V} = Q \cdot 0.6V = -18fJ$$

(Charge flows in to 0.6V supply, so energy is indeed returned to that supply.)

$$E_{inverter} = E_{1.2V} + E_{0.6V}$$

$$E_{inverter} = 18fJ$$