

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering and Computer Sciences**

EECS 40  
Introduction to Microelectronic Circuits

Fall 2003

**MIDTERM EXAMINATION #1**  
September 29, 2003  
Time allotted: 50 minutes

**NAME:** \_\_\_\_\_, \_\_\_\_\_  
(print) **Last** **First**

**Signature:** \_\_\_\_\_ **STUDENT ID#:** \_\_\_\_\_

**Discussion Section:** \_\_\_\_\_ [1 pt]

1. This is a **CLOSED BOOK** exam. However, you may use 1 page of notes and a calculator.
2. **SHOW YOUR WORK** on this exam. (Make your methods clear to the grader.)
3. **Write your answers clearly in the spaces (lines, boxes, or plots) provided.**
4. Remember to specify the units on answers whenever appropriate.

**SCORE:**    1 \_\_\_\_\_ / 15


                  2 \_\_\_\_\_ / 20

                  3 \_\_\_\_\_ / 14

**Total:**    \_\_\_\_\_ / 50


**Problem 1: Circuit Analysis [15 points in total]**

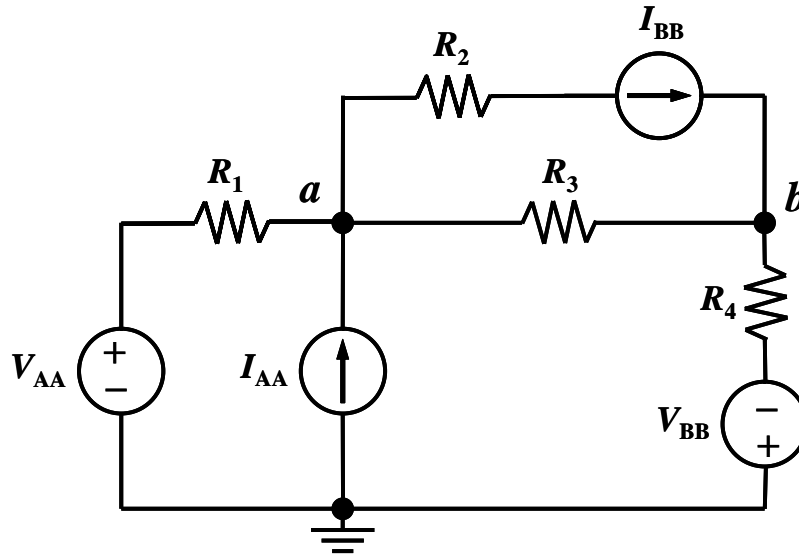- a) In the circuit below, the independent source values and resistances are known. Use the node-voltage method to write 2 equations sufficient to solve for  $V_a$  and  $V_b$ . To receive credit, you must write your answer in the box below. [5 pts]  
DO NOT SOLVE THE EQUATIONS!




Write your equations here:

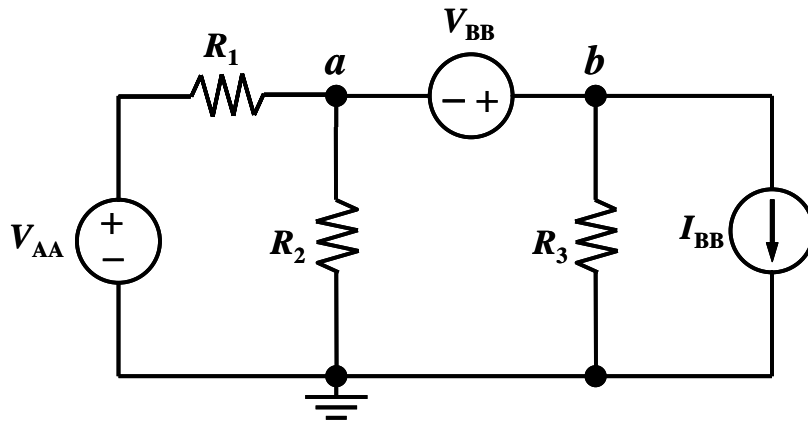- b) In the circuit below, the independent source values and resistances are known. Use the node-voltage method to write 2 equations sufficient to solve for  $V_a$  and  $V_b$ . To receive credit, you must write your answer in the box below. [5 pts]  
DO NOT SOLVE THE EQUATIONS!



Write your equations here:

c) Find  $V_o$ . [5 pts]

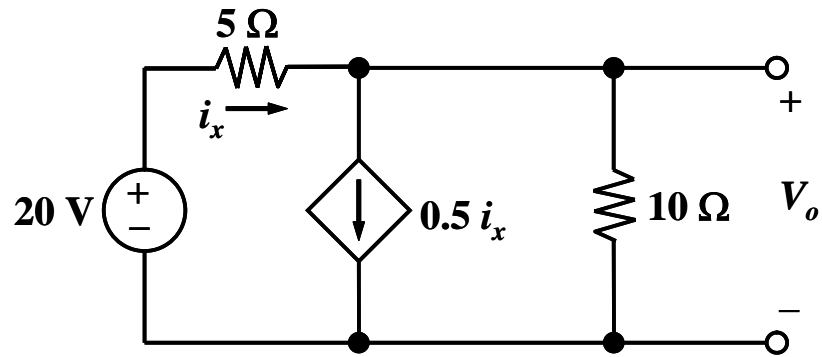

$V_o =$  \_\_\_\_\_

**Problem 2: Equivalent Circuits [20 points in total]**

a) Suppose you are given five resistors, each of value  $10\text{ k}\Omega$ .



- i) What is the **maximum resistance** which can be achieved by connecting these five resistors? Show how they should be connected in this case. [3 pts]

Circuit diagram of resistors connected to give a **maximum resistance value** of \_\_\_\_\_  $\Omega$ :

- ii) What is the **minimum resistance** which can be achieved by connecting these five resistors? Show how they should be connected in this case. [3 pts]



Circuit diagram of resistors connected to give a **minimum resistance value** of \_\_\_\_\_  $\Omega$ :

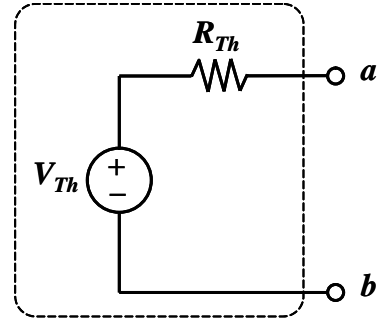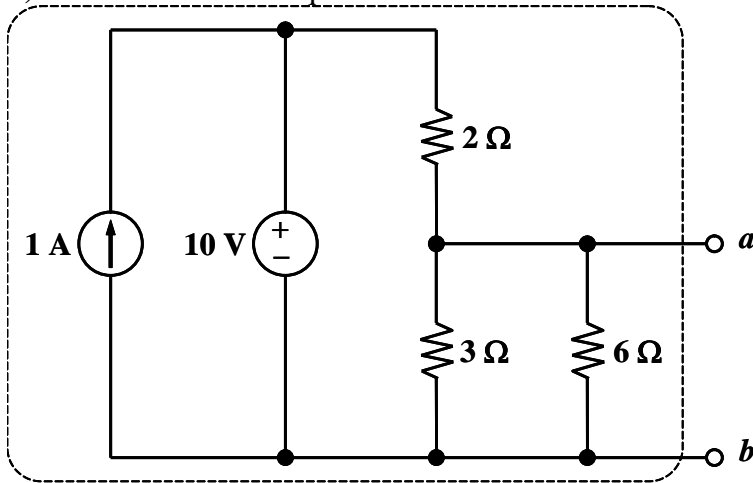b) Find the Thévenin equivalent circuit for the circuit below. [8 pts]



|                  |
|------------------|
| $V_{Th} =$ _____ |
| $R_{Th} =$ _____ |

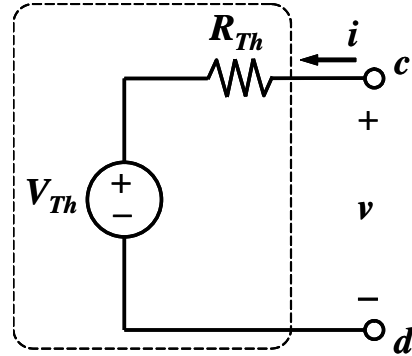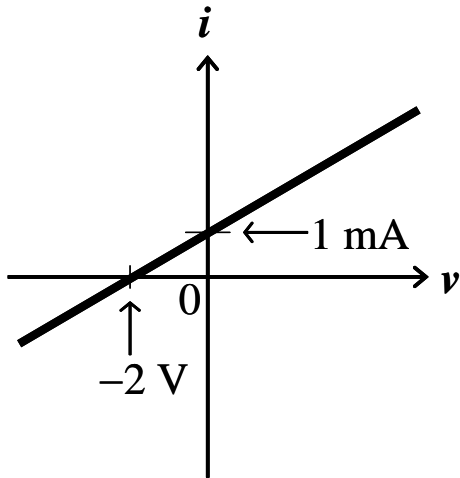- c) The  $I$ - $V$  characteristic of a linear circuit is given below. Find the Thévenin equivalent of this circuit. [3 pts]



$$V_{Th} = \underline{\hspace{10em}}$$


$$R_{Th} = \underline{\hspace{10em}}$$

- d) Suppose the circuit in part (c) is loaded with a resistor of resistance  $R_L$  (connected between terminals  $c$  and  $d$ ). What is the maximum power that can be delivered to this load resistor? [3 pts] (Hint: You should choose the value of  $R_L$  which results in the maximum power absorbed by the load resistor, and then calculate that power.)

$$P_{max} = \underline{\hspace{10em}}$$

**Problem 3: Op Amp Circuit [14 points in total]**

Consider the op amp circuit below:

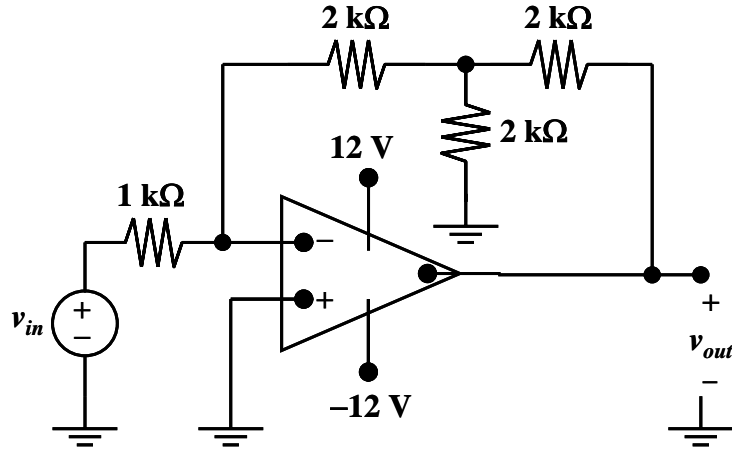

- a) Assuming the op amp is operating in its linear region, find an expression for  $v_{out}$  (as a function of  $v_{in}$ ). [10 pts]

$$v_o = \underline{\hspace{10em}}$$

- b) Sketch the voltage transfer characteristic for the op-amp circuit, for  $v_{in}$  ranging from  $-5$  Volts to  $+5$  Volts. Indicate the minimum and maximum values of  $v_{out}$ . [4 pts]

